

Basic Input Circuits


Prof. Dr. M. Zahurul Haq
zahurul@me.buet.ac.bd
http://teacher.buet.ac.bd/zahurul/

Department of Mechanical Engineering
Bangladesh University of Engineering & Technology

ME 361: Instrumentation & Measurement



Current-sensitive Input Circuit

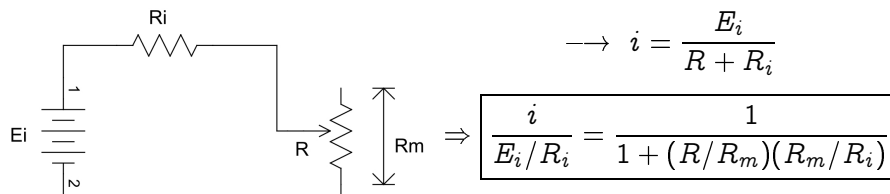

f001.eps

- Current flow through the circuit indicates sensor's resistance R .
- Current flow varies linearly with R for some ranges of operation.




Basic Input Circuits

Most common input circuits used in transducer work:

- 1 Current-sensitive Circuit
- 2 Voltage-sensitive (ballast) Circuit
- 3 Voltage-divider Circuit
- 4 Voltage-balancing Potentiometer Circuit
- 5 Bridge Circuit
- 6 Amplifier Circuit



Voltage-sensitive (ballast) Circuit

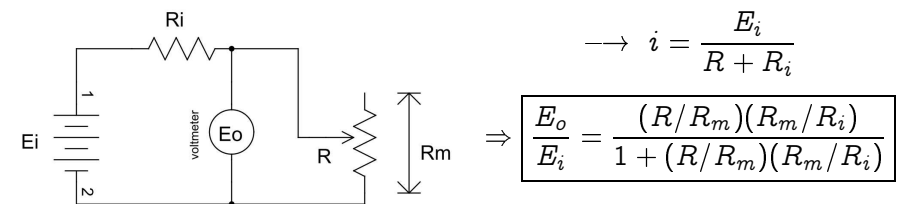


f002.eps

- Voltmeter impedance is very high & draws negligible current.
- Change in R is indicated by voltage change.
- Sensitivity, $S = \frac{dE_o}{dR} = \frac{E_i R_i}{(R + R_i)^2}$
- For maximum sensitivity, $\frac{dS}{dR_i} = 0 = \frac{E_i(R - R_i)}{(R + R_i)^3} \Rightarrow R_i = R$

↪ Homework: Example 4.1 (Holman)



Voltage-divider Circuit

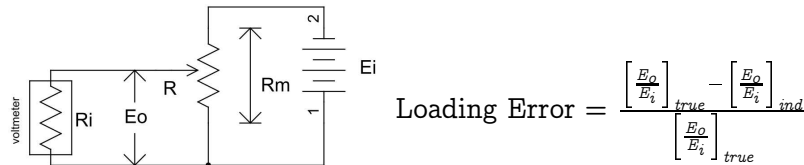

$$\text{Loading Error} = \frac{\left[\frac{E_o}{E_i}\right]_{\text{true}} - \left[\frac{E_o}{E_i}\right]_{\text{ind}}}{\left[\frac{E_o}{E_i}\right]_{\text{true}}}$$

f003.eps


- Source voltage E_i is impressed across the total transducer resistance R_m , while the variable contact is connected to a voltmeter with internal resistance R_i .

- For $R_i \gg R_m$: $\Rightarrow \left[\frac{E_o}{E_i}\right]_{\text{true}} = \frac{R}{R_m}$

- For $R_i \ll R_m$: $\Rightarrow \left[\frac{E_o}{E_i}\right]_{\text{ind}} = \frac{R/R_m}{1 + (R/R_m)(1 - R/R_m)(R_m/R_i)}$

\rightsquigarrow Homework: Example 4.2 (Holman)

Wheatstone Bridge Circuit

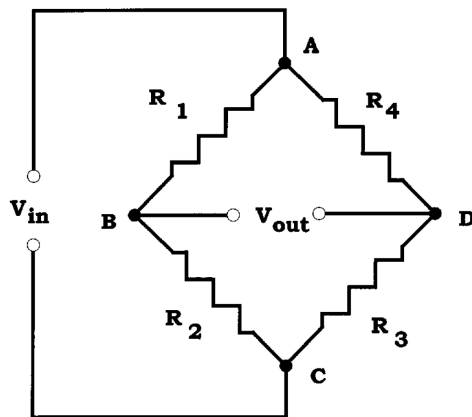


$$V_B = V_{in} \frac{R_2}{R_1 + R_2}$$

$$V_D = V_{in} \frac{R_3}{R_3 + R_4}$$

$$V_{out} = V_B - V_D$$

e671.eps

Voltage-balancing Potentiometer Circuit

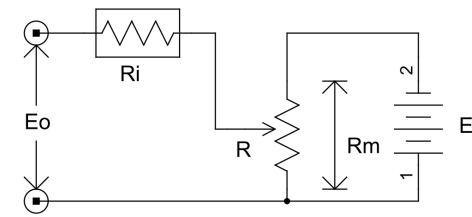

f004.eps

- Used for precise measurements of small electrical potentials by comparison, particularly those generated by thermocouples.
- A known portion of source voltage E_i is balanced against the unknown voltage E_o through the use of a variable resistor R_m .
- At balance point, current through the galvanometer is zero. $\Rightarrow \frac{E_o}{E_i} = \frac{R}{R_m}$
- Galvanometer resistance R_i does not effect the reading.
- Source voltage E_i must be accurately known to determine E_o .

Null Method:

- $V_{out} = 0 \rightarrow i_g = 0 \Rightarrow \frac{R_2}{R_1} = \frac{R_3}{R_4}$
- If the resistor R_2 varies with changes in the measured physical variable, one of the other arms of the bridge can be adjusted to null the circuit and determine the resistance. The balancing mechanism may be accomplished manually or automatically through a closed loop controller circuit. The values of the other resistors must be precisely known.

Deflection Method:

- Used for dynamic signals where time is insufficient for balancing.
- Galvanometer/detector deflection indicates the deviation at one of the arms (transducer arm) from some balanced condition.
- Bridge output may be measured by:
 - Low-impedance device \rightsquigarrow Current-sensitive circuit.
 - High-impedance device \rightsquigarrow Voltage-sensitive circuit.

WB Circuit: Deflection Method

Voltage-sensitive Circuit: V_{out} is measured by high impedance device. At balanced condition, $V_{out} = 0$. If $R_2 \rightarrow R_2 + \Delta R_2$.
 $\Rightarrow \frac{V_{out}}{V_{in}} = \frac{R_2 + \Delta R_2}{R_1 + R_2 + \Delta R_2} - \frac{R_3}{R_3 + R_4} = \frac{\Delta R_2/R}{4 + 2(\Delta R_2/R)} \leftarrow R_1 = \dots = R_4 = R$

Current-sensitive Circuit: i_g is measured by galvanometer with R_g .
 $\Rightarrow i_g = \frac{V_{out}}{R_{TH} + R_g} = \frac{V_{out}}{C} (R_2 R_4 - R_1 R_3)$

$$C = R_1 R_2 (R_3 + R_4) + R_3 R_4 (R_1 + R_2) + R_g (R_1 + R_2 + R_3 + R_4)$$

At null position $\Rightarrow R_2 R_4 = R_1 R_3 : i_g = 0$


If transducer resistance, $R_2 \rightarrow R_2 + \Delta R_2 \Rightarrow i_g \rightarrow \Delta i_g$.

$$\Rightarrow \Delta i_g = \frac{V_{out}}{C} [(R_2 + \Delta R_2) R_4 - R_1 R_3] = \frac{V_{out}}{C} R_4 \Delta R_2$$

↪ Homework: Example 4.4, 10.6 & 10.7 (Holman)

↪ Homework: Example 6.4 & 6.5 (Figliola)

Strain Gauge using Wheatstone Bridge

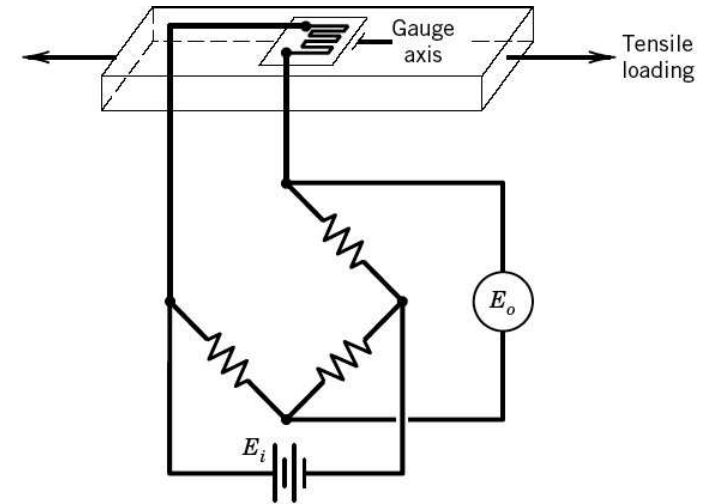

e677.eps