

# Digital Electronics


Prof. Dr. M. Zahurul Haq  
 zahurul@me.buet.ac.bd  
<http://teacher.buet.ac.bd/zahurul/>

Department of Mechanical Engineering  
 Bangladesh University of Engineering & Technology

ME 475: Mechatronics




## AND Gate

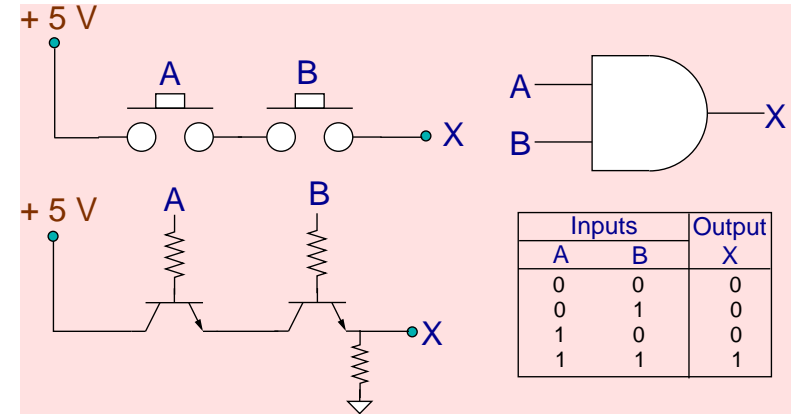

- Output, X, is HIGH only if inputs A and B are both HIGH.
- Boolean Equation:  $X = A \text{ AND } B = A \cdot B = AB$




... contd.

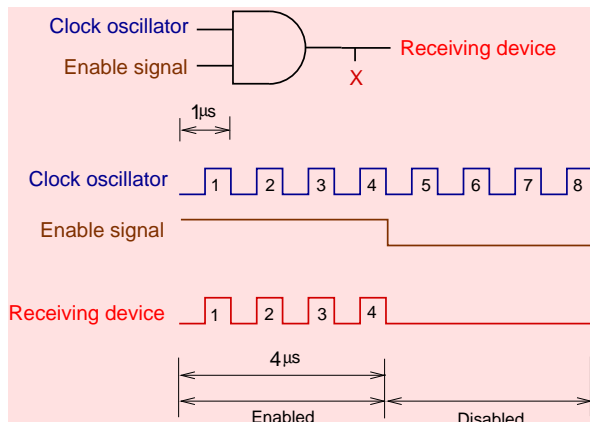

- AND gate can be used to enable a waveform to transmit from one point to another. The LOW value disables the clock from reaching the X-output.




## OR Gate

 

- Output, X, is HIGH if input A or input B is HIGH or both are HIGH.
- Boolean Equation:  $X = A \text{ OR } B = A + B$



... contd.

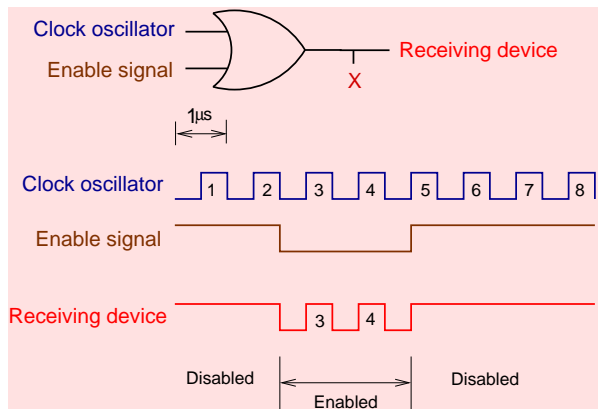


- OR gate can be used to **disable** a waveform from transmitting from one point to another.



 
## NAND & NOR Gates

- NAND:** Boolean Equation:  $X = \overline{AB}$
- Output is always HIGH unless both inputs are HIGH.




 - NOR:** Boolean Equation:  $X = \overline{A + B}$
- Output is always LOW unless both inputs are LOW.



 
## Buffer & Inverter ICs

- Buffer IC:** Boolean Equation:  $X = A$



 - Inverter IC:** Boolean Equation:  $X = \overline{A}$



## Ex-OR/Ex-NOR Gates

- Exclusive-OR (Ex-OR) gate provides a HIGH output if one input or the other input is HIGH, but not the both.

$$\text{Ex-OR: } X = A \oplus B = \overline{A}B + A\overline{B}$$

- Ex-NOR is the complement of the Ex-OR. It provides a HIGH output for both inputs HIGH or both inputs LOW.


$$\text{Ex-NOR: } X = \overline{A \oplus B} = AB + \overline{A}\overline{B}$$

A	B	X(OR)	X(Ex-OR)	X(Ex-NOR)
0	0	0	0	1
0	1	1	1	0
1	0	1	1	0
1	1	0	0	1



 
## Parity Generator/Checking



- In digital data transmission external noise can cause an error. Parity system is used to recognise the error and take corrective measures (retransmission).
- Parity system puts an extra bit to the digital transmission.
- odd parity: sum of all bits is odd.
- even parity: sum of all bits is even.



## Combinational Logic Example

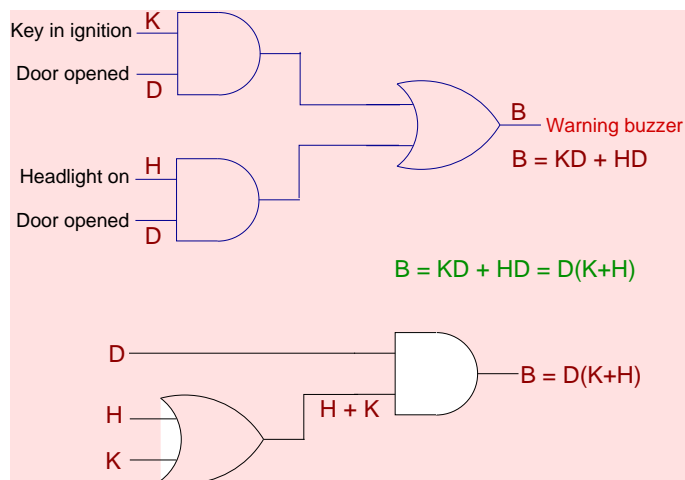

## ... contd.

  

$I_0 - I_8$	$\Sigma_E$	$\Sigma_O$
Even	HIGH	LOW
Odd	LOW	HIGH



## Boolean Algebra Laws

- Commutative law of addition:  $A + B = B + A$ , and multiplication:  $AB = BA$ .  
These laws mean that the order of ORing and ANDing does not matter.
- Associative law of addition:  $A + (B + C) = (A + B) + C$ , and multiplication:  $A(BC) = (AB)C$ .  
These laws mean that the grouping of several variables ORed or ANDed together does not matter.
- Distributive law:  $A(B + C) = AB + BC$ , and  $(A + B)(C + D) = AC + AD + BC + BD$ .  
These laws show methods for expanding an equation containing ORs and ANDs.




## Boolean Algebra Rules

- ① Anything ANDed with a 0 is equal to 0 ( $A \cdot 0 = 0$ ).
- ② Anything ANDed with a 1 is equal itself ( $A \cdot 1 = A$ ).
- ③ Anything ORed with a 0 is equal itself ( $A + 0 = A$ ).
- ④ Anything ORed with a 1 is equal to 1 ( $A + 1 = 1$ ).
- ⑤ Anything ANDed with itself is equal itself ( $A \cdot A = A$ ).
- ⑥ Anything ORed with itself is equal itself ( $A + A = A$ ).
- ⑦ Anything ANDed with its own compliment equals 0 ( $A \cdot \bar{A} = 0$ ).
- ⑧ Anything ORed with its own compliment equals 1 ( $A + \bar{A} = 1$ ).
- ⑨ A variable that is complemented twice will return to its original logic level ( $\bar{\bar{A}} = A$ ).
- ⑩ (a)  $A + \bar{A}B = A + B$   
 (b)  $\bar{A} + AB = \bar{A} + B$



 
## Reduction of Logic Circuits: Example 2



$$\begin{aligned}
 X &= [(A + \bar{B})(B + C)]B \\
 &= (AB + AC + \bar{B}B + \bar{B}C)B \quad \text{Law 3} \\
 &= (AB + AC + 0 + \bar{B}C)B \quad \text{Rule 7} \\
 &= (AB + AC + \bar{B}C)B \quad \text{Rule 3} \\
 &= ABB + ACB + \bar{B}CB \quad \text{Law 3} \\
 &= ABB + ABC + \bar{B}BC \quad \text{Law 1} \\
 &= AB + ABC = AB(1 + C) \quad \text{Rule 5, 7 \& 1; \& then factorisation} \\
 &= AB \quad \text{Rule 2}
 \end{aligned}$$


 
## Reduction of Logic Circuits: Example 1




$$\begin{aligned}
 X &= (A + B)\bar{B} + \bar{B} + BC \\
 &= A\bar{B} + B\bar{B} + \bar{B} + BC \quad \text{Law 3} \\
 &= A\bar{B} + 0 + \bar{B} + BC \quad \text{Rule 7} \\
 &= A\bar{B} + \bar{B} + BC \quad \text{Rule 3} \\
 &= \bar{B}(A + 1) + BC \quad \text{Factorisation} \\
 &= \bar{B} \cdot 1 + BC \quad \text{Rule 4} \\
 &= \bar{B} + BC \quad \text{Rule 2} \\
 &= \bar{B} + C \quad \text{Rule 10(b)}
 \end{aligned}$$


 
## De Morgan's Theorem 1

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$



A	B	$X = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0


A	B	$X = \bar{A} + \bar{B}$
0	0	1
0	1	1
1	0	1
1	1	0

← Equivalent Result →



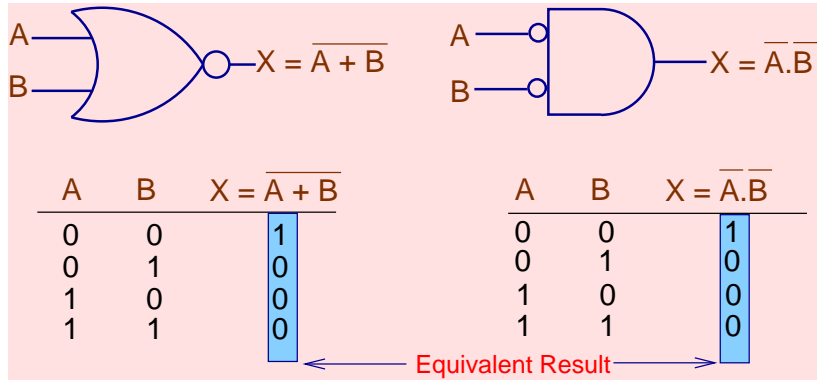
## De Morgan's Theorem 2

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



## De Morgan's Theorem: Application

 


$$\begin{aligned}
 X &= \overline{\overline{A} \cdot \overline{B} + \overline{C}} \\
 &= \overline{(\overline{A} + \overline{B}) \cdot \overline{C}} \\
 &= \overline{\overline{A} \cdot \overline{B} \cdot \overline{C}} + \overline{\overline{B} \cdot \overline{B} \cdot \overline{C}} \\
 &= \overline{\overline{A} \cdot \overline{B} \cdot \overline{C}} + \overline{\overline{B} \cdot \overline{C}} \\
 &= \overline{\overline{B} \cdot \overline{C}(\overline{A} + 1)} \\
 &= \overline{\overline{B} \cdot \overline{C}} \\
 &= \overline{\overline{B + C}}
 \end{aligned}$$

De Morgan's theorem




## De Morgan's Theorem: Application

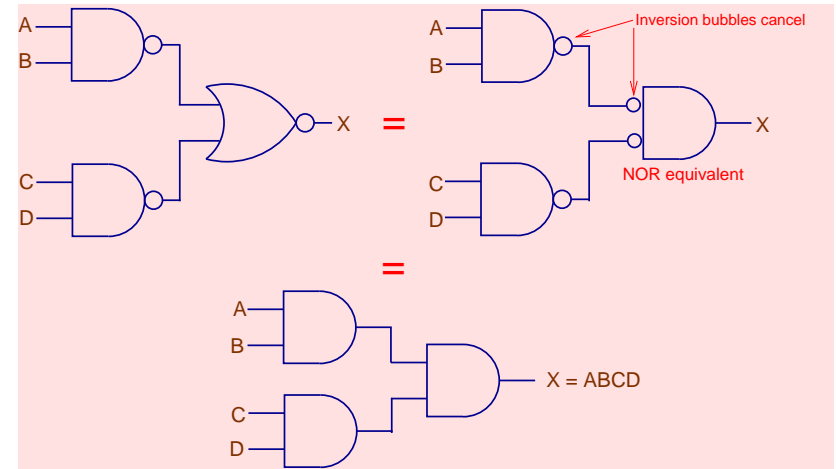

## Binary Addition of LSB

$$A_o + B_o = \Sigma_o + C_{out}$$

A <sub>o</sub>	B <sub>o</sub>	Σ <sub>o</sub>	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

- Addition of binary & decimal numbers are similar. The binary sum is made up of only 1's and 0's.
- For LSB bit, half adder (HA) circuit is used which does not have a carry-in bit from a previous digit.
- In other bits, if a carry-out is produced, it is added to the next-more-significant column as carry-in, C<sub>in</sub>.



... contd.


$C_{in}$	$C_{in}$				
$A_1$	$A_0$				
$B_1$	$B_0$				
$\Sigma_1$	$\Sigma_0$				
$C_{out}$	$C_{out}$				
$A_1$	$B_1$	$C_{in}$	$\Sigma_1$	$C_{out}$	
0	0	0	0	0	
0	0	1	1	0	
0	1	0	1	0	
0	1	1	0	1	
1	0	0	1	0	
1	0	1	0	1	
1	1	0	0	1	
1	1	1	1	1	

Decimal	Binary
31	0001 1111
+7	+0000 0111
38	0010 0110




## Binary Addition

contd.

 

Logic diagram of a full-adder.

 


Block diagram of a 4-bit binary adder.



 
## Comparators

- The basic comparator evaluates two binary strings bit by bit and outputs 1 if they are exactly the same.
- Ex-NOR is the easiest way to compare equality of bits.


 
## Combinational vs. Sequential Logic

- In combinational logic ckt, state depends upon the actual signals being applied to their inputs at that time.
- Sequential logic circuits have some form of inherent memory and these are able to take into account their previous input state as well as those actually present.
- Sequential logic ckts can be divided into 3 main groups:
  - 1 Clock driven: ckts are synchronised to specific CLK signal.
  - 2 Even driven: asynchronous ckts to react when external event occurs.
  - 3 Pulse driven: combination of synchronous & asynchronous.




- +ve edge trigger devices respond to low-to-high transition.
- ve edge trigger devices respond to high-to-low transition.



 
# S-R Flip-Flop

- SR flip-flop be constructed using two NOR or NAND gates.
- $S = 1, R = 0 \implies Q = 1 \text{ \& } \bar{Q} = 0$ : Set condition.
- $S$  removed:  $S = 0, R = 0 \implies Q = 1 \text{ \& } \bar{Q} = 0$ : Hold.
- $S = 0, R = 1 \implies Q = 0 \text{ \& } \bar{Q} = 1$ : Reset
- $S = 1, R = 1$ : Not used.



S	R	Q
0	0	Present state
0	1	Reset
1	0	Set
1	1	Disallowed

S	R	Q
1	0	1
0	0	1
0	0	1
0	1	0
0	0	0
0	0	0
0	1	0
0	0	0
1	0	1
0	0	1

 


e587 . eps

e588 . eps




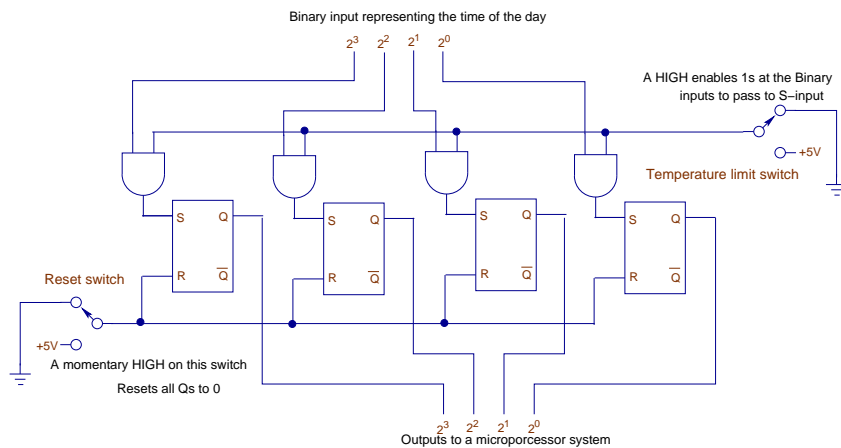
# ... Applications

To register the binary value representing the time when a temperature limit switch goes into a HIGH.




# ... contd.

  
 
# ... Switch Bounce & De-bouncer

When switches are opened or closed, there are brief current oscillations due to mechanical bouncing or electrical arcing.




e586 . eps

e291 . eps



## Gated S-R Flip Flop

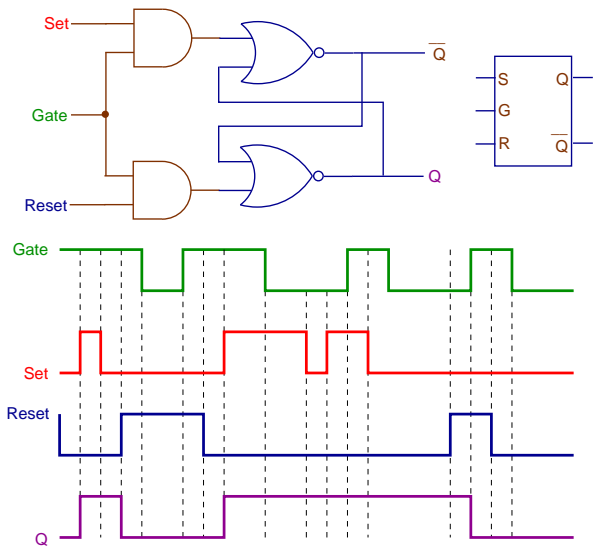

... contd.

- Level-triggered devices respond to their inputs while the clock signal is at a high level and retain their output values after the level changes.
- The output  $Q$  tracks the input  $D$  while  $CK$  is high. At the negative edge (i.e. when  $CK$  goes low), the flip-flop output will hold or latch the value  $D$  had at the edge transition.


$D$	$CK$	$Q$	$\bar{Q}$
0	1	0	1
1	1	1	0
$x^1$	0	$Q_o$	$\bar{Q}_o$

<sup>1</sup>the value of  $D$  has no effect on the output as long as  $CK$  is low


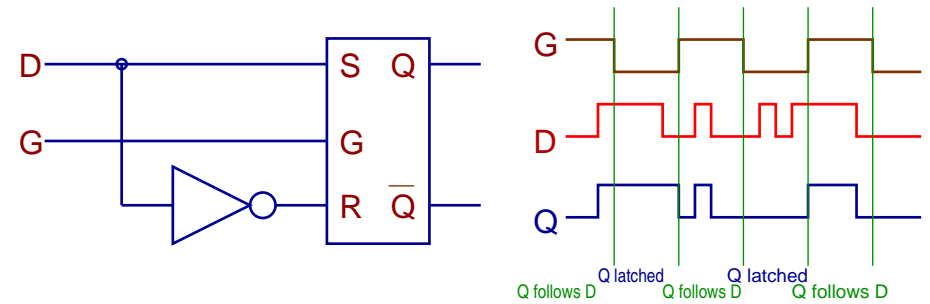
## Data Latch


A level-triggered flip-flop is a latch. Data latch can be formed from the gated S-R Flip-flop by the addition of an inverter; this enables just a single input ( $D$ ) to latch the previous input value.



## D Flip-Flop


- It has a single input  $D$  whose value is stored and presented at the output  $Q$  at the +ve or -ve edge of  $CLK$ .

$D$	$CK$	$Q$	$\bar{Q}$
0	↑	0	1
1	↑	1	0
$x$	0	$Q_o$	$\bar{Q}_o$
$x$	1	$Q_o$	$\bar{Q}_o$

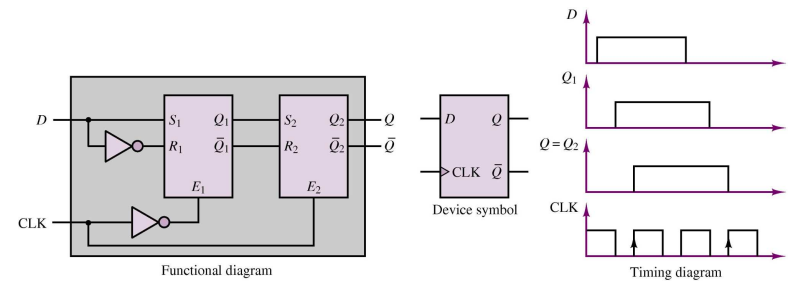




## JK Flip-flop

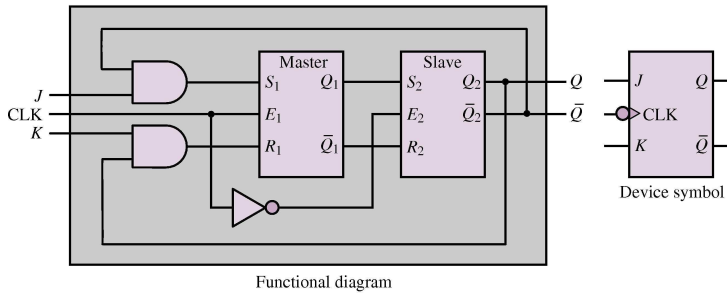

- When J and K are both low, no change in state occurs.
- When J = 0 and K = 1, the flip-flop is reset to 0.
- When J = 1 and K = 0, the flip-flop is set to 1.
- When both J and K are high, the flip-flop will toggle between states at every -ve edge of CLK.




## 3-bit Binary Counter

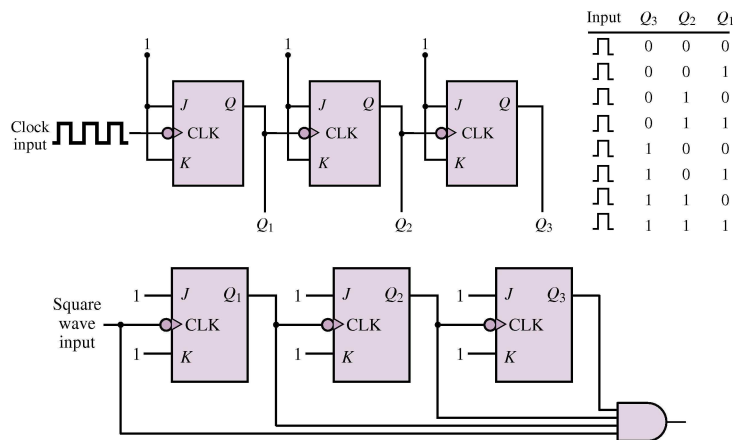

A 3-bit ripple counter can be configured as a divide-by-8 mechanism simply by adding an AND gate.




## T Flip-flop

 

T flip-flop is a JK flip-flop with its inputs tied together. It toggles between the high and low state at half of the clock frequency. It can be used as a *divide by 2 counter*.



## 4-bit Binary Counter

 


The ckt may be used as a frequency divider. Output  $B_0$ ,  $B_1$ ,  $B_2$ ,  $B_3$  are divide by -2, -4, -8 & -16 outputs, respectively.



## Decade Counter


Input pulses	$b_3$	$b_2$	$b_1$	$b_0$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0

 

A decade counter counts from 0 to 9 and then resets.




## Cascaded Decade Counter

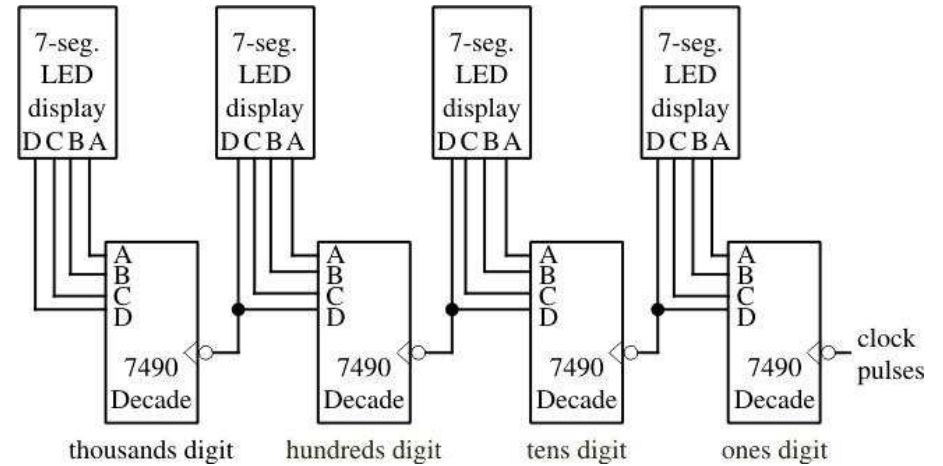

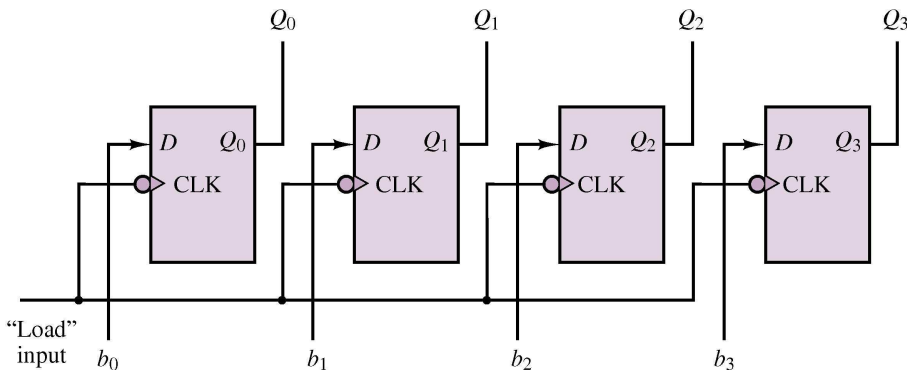
## 4-bit Parallel Register

In the register, the *load input pulse acts on all clocks simultaneously causing the parallel inputs to be transferred to the respective flip-flops to store the binary data.*



## 4-bit Shift Register

 

Same basic structure of parallel register applies to the shift register, except that the input is now applied to the first flip-flop and shifted along at each clock pulse. Note that, this type of register provides both a serial and a parallel output.

