

Operational Amplifier (Op-Amp)

The OP-Amp is a low-cost and versatile IC (Integrated Circuit) consisting of many internal transistors, resistors, and capacitors. These are basic building blocks for:

- Amplifiers
- Integrators and Differentiators
- Summers
- Comparators
- A/D and D/A converters
- Active filters
- Sample and Hold circuits
- . . . etc.

Operational Amplifiers

Prof. Dr. M. Zahurul Haq
zahurul@me.buet.ac.bd
<http://teacher.buet.ac.bd/zahurul/>

Department of Mechanical Engineering
Bangladesh University of Engineering & Technology


ME 475: Mechatronics




OP-Amp: Components

The OP-Amp has **Single Output** and **Two Inputs**:

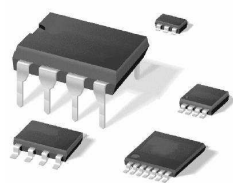
- 1 Noninverting input [+]: output is in phase with input.
- 2 Inverting input [-]: output is 180° out of phase with input.



(a)

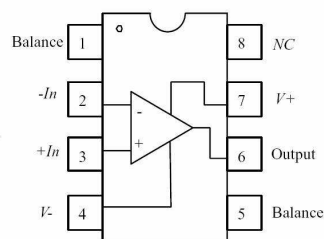

(b)

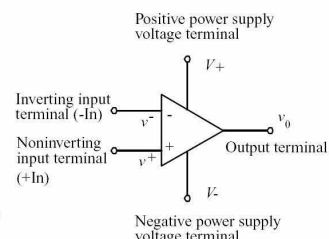

(c)




Operational Amplifier (Op-Amp)

The OP-Amp is a low-cost and versatile IC (Integrated Circuit) consisting of many internal transistors, resistors, and capacitors. These are basic building blocks for:

- Amplifiers
- Integrators and Differentiators
- Summers
- Comparators
- A/D and D/A converters
- Active filters
- Sample and Hold circuits
- . . . etc.



Internal Design of LM741

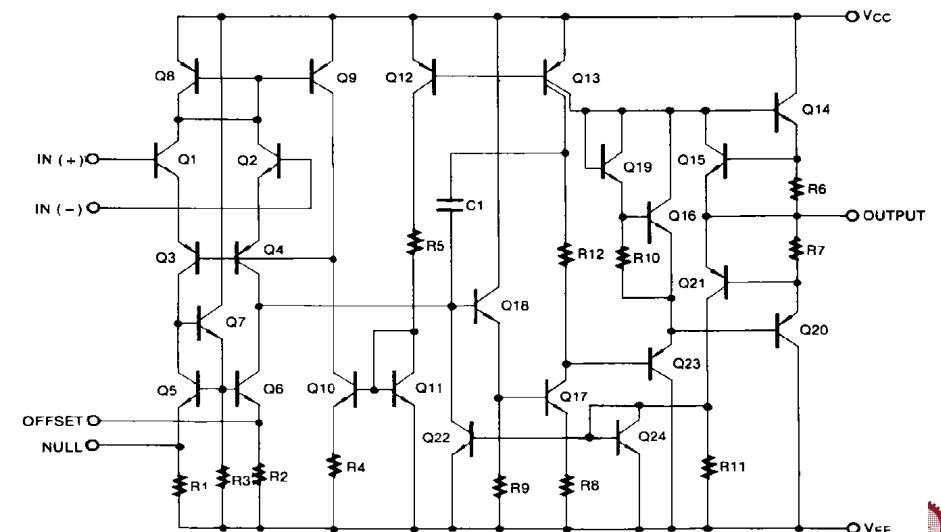


OP-Amp: Equivalent Circuit

Rule 1. Infinite input impedance, $Z_{in} = \infty \implies I_+ = I_- = 0$;


Rule 2. Infinite gain, $\implies E_+ = E_-$;

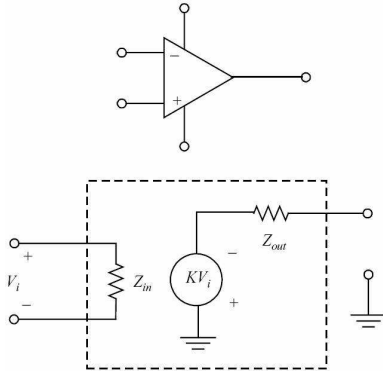Rule 3. Zero output impedance, $Z_{out} = 0 \implies E_o \neq f(I_o)$.




e427.eps

OP-Amp: Examples

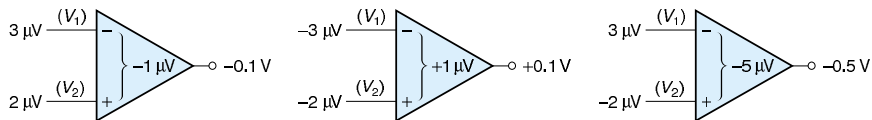

e176.eps

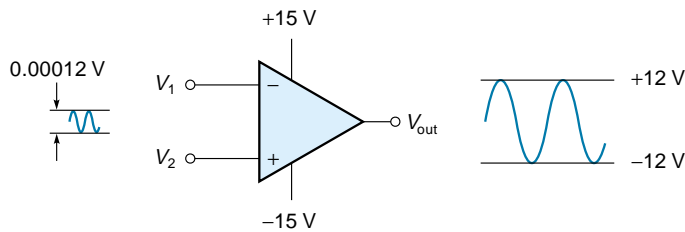


e177.eps

OP-Amp: Characteristics

Characteristics	Ideal Value	Typical real-world value
Open-loop gain	∞	$10^5 V/V$
Offset voltage	0	$\pm 1 mV$
Bias currents	0	$10^{-6} - 10^{-14} A$
Input impedance	∞	$10^5 - 10^{11} \Omega$
Output impedance	0	$1 - 10 \Omega$

- Ideal op-amps rejects inputs common to both inputs (common mode rejection).
- Actual Common Mode Rejection Ratio, $CMRR = \frac{E_o/E_i}{E_o/E_{cm}} \geq 10^6$
the larger the CMRR, the better the amplifier.

OP-Amp: Voltage Comparator

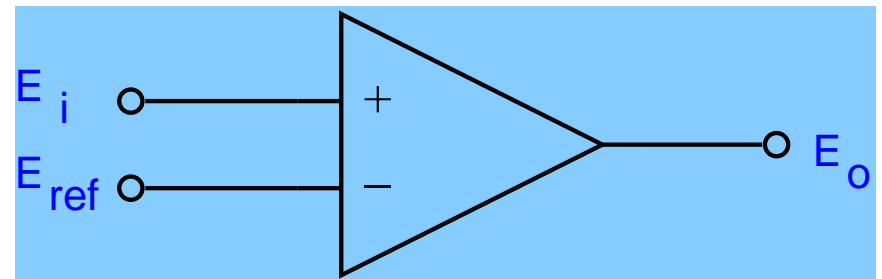


x007.eps

In comparator circuit, there is no negative feedback, hence the circuit exhibits infinite gain and the op-amps will saturate, i.e. the output remains at the most positive or most negative output value. Hence,

$$E_o = \begin{cases} +E_{sat} & E_i > E_{ref} \\ -E_{sat} & E_i < E_{ref} \end{cases}$$

Comparator Circuit: Application

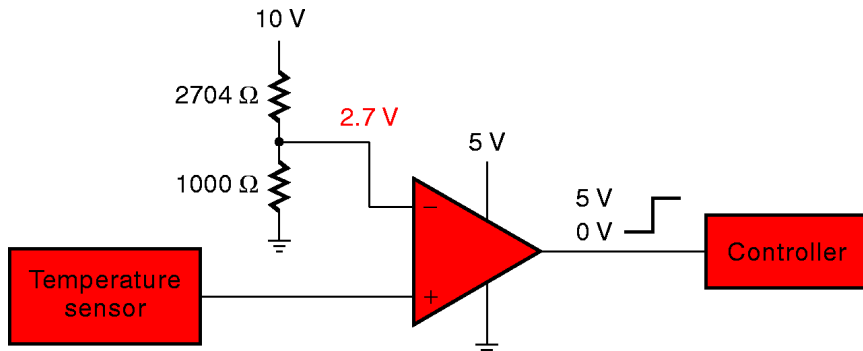


e040.eps

Chatter is a practical problem, output voltage oscillates back-and-forth when input voltage is near to the threshold.



Window Comparator Circuit

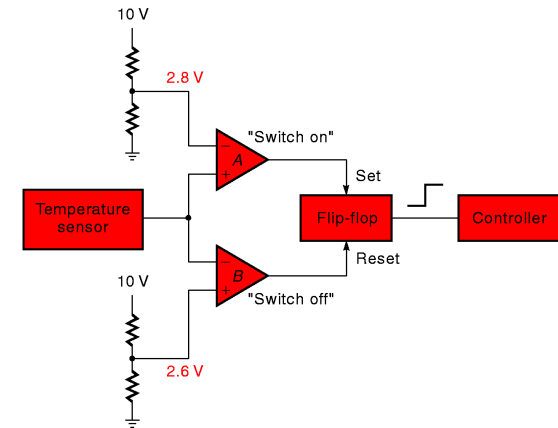


e041.eps

Window Comparator is with inbuilt hysteresis; hysteresis means that switch-on voltage is greater than switch-off voltage.



OP-Amp: Inverting Amplifier

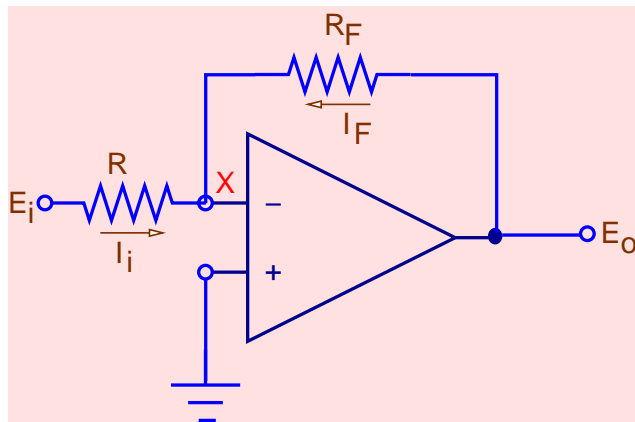


x008.eps

At X, $I_i + I_F = 0$ (KCL & Rule 1), & $E_X = 0$ (Rule 2);

$I_i \left(\equiv \frac{E_i - E_X}{R} \right) = -I_F \left(\equiv \frac{E_o - E_X}{R_F} \right) \implies \text{gain, } G = \frac{E_o}{E_i} = -\frac{R_F}{R}$



OP-Amp: Noninverting Amplifier

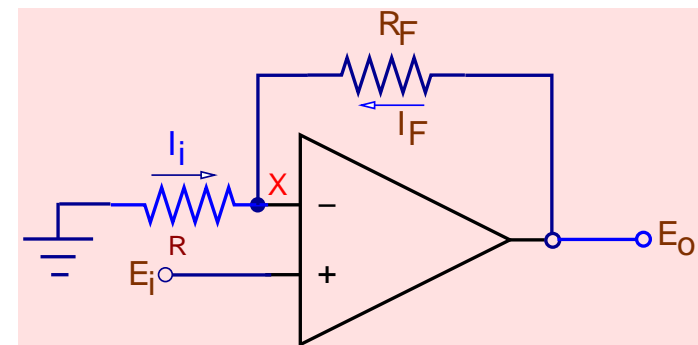

x009.eps


At X, $I_i + I_F = 0$ (KCL & Rule 1), & $E_X = E_i$ (Rule 2);

$I_i \left(\equiv \frac{-E_X}{R} \right) = -I_F \left(\equiv \frac{E_o - E_X}{R_F} \right) \implies G = 1 + \frac{R_F}{R}$





OP-Amp: Follower/Buffer

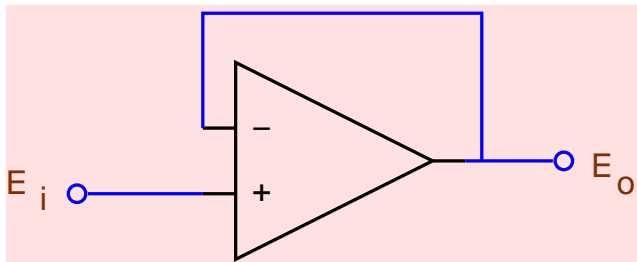- In a noninverting amplifier with $R = \infty$ & $R_F = 0$, gain, G is unity and there is no voltage amplification. This circuit is known as a *buffer* or *follower*.
- It has a high input impedance and low output impedance. The high input impedance effectively isolates the source from the rest of the circuit.




x010.eps


Op-Amp: Voltage Follower Application

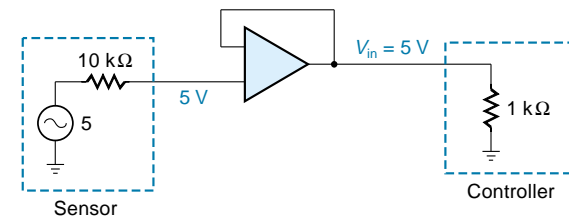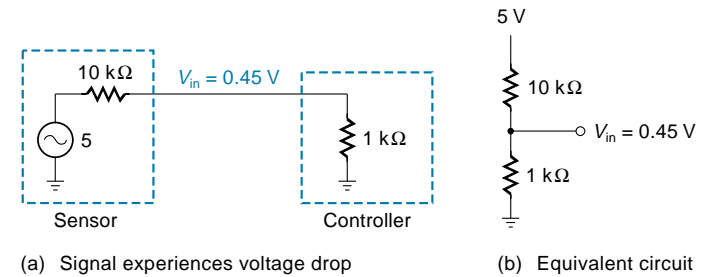

Op-Amp: Summing Amplifier

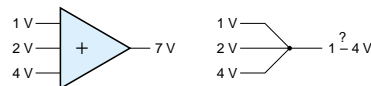

e179.eps

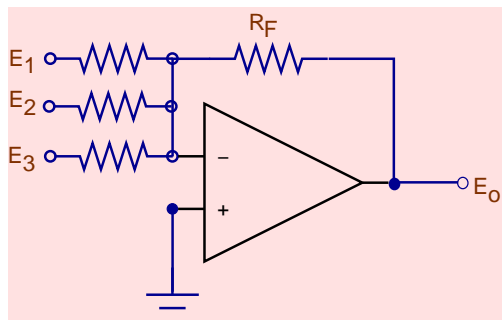


x011.eps

$$E_o = -R_F \left[\frac{E_1}{R_1} + \frac{E_2}{R_2} + \frac{E_3}{R_3} \right]$$

Summing Amplifier: Application

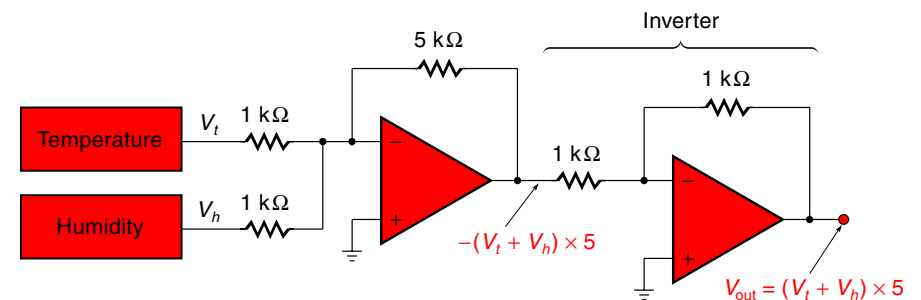
Example: Interface circuit for an air conditioning system

- when the sum of the voltages of temperature and humidity sensors goes above 1.0 V, &
- a threshold circuit in air conditioner require 5.0 V.



e042.eps

OP-Amp: Differential Amplifier

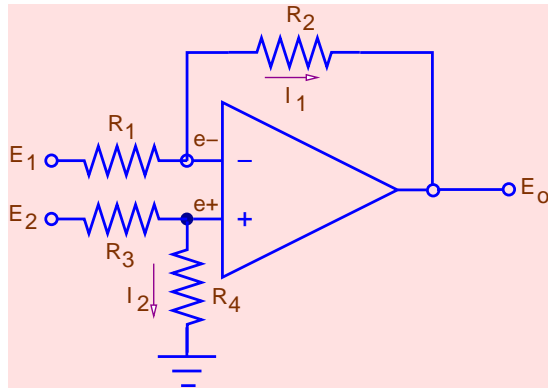

x012.eps


$$e^- = e^+ \Rightarrow E_1 \left[\frac{R_2}{R_1 + R_2} \right] + E_o \left[\frac{R_1}{R_1 + R_2} \right] = E_2 \left[\frac{R_4}{R_3 + R_4} \right]$$

$$E_o = E_2 \left[\frac{R_4}{R_3 + R_4} \cdot \frac{R_1 + R_2}{R_1} \right] - E_1 \left[\frac{R_2}{R_1} \right]$$

$$E_o = (E_2 - E_1) \left[\frac{R_2}{R_1} \right] = c(E_2 - E_1) \text{ if } \frac{R_2}{R_1} = \frac{R_4}{R_3} = c$$



Instrument Amplifier

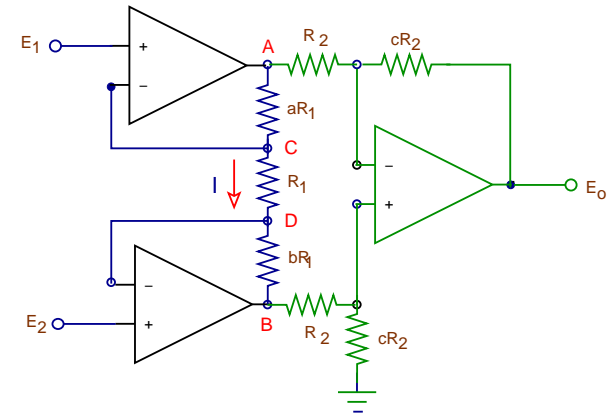


x013.eps

$$I = \frac{E_c - E_D}{R_1} = \frac{E_1 - E_2}{R_1} = \frac{E_A - E_B}{aR_1 + R_1 + bR_1}; \quad \& \quad E_o = c(E_A - E_B)$$

$$G = \frac{E_o}{E_2 - E_1} = c(1 + a + b)$$




OP-Amp: Integrator

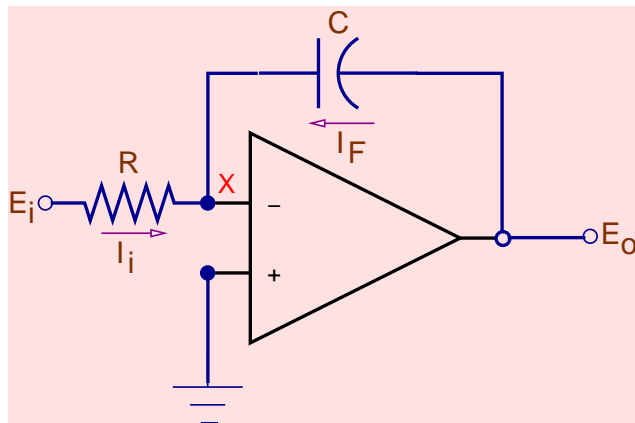

x014.eps


$$I_i = C \frac{E_i}{R}, \quad I_F = c \frac{dE_o}{dt} \quad \& \quad I_i + I_F = 0 \text{ (KCL)}$$

$$E_o = -\frac{1}{RC} \int E_i(\tau) d\tau$$

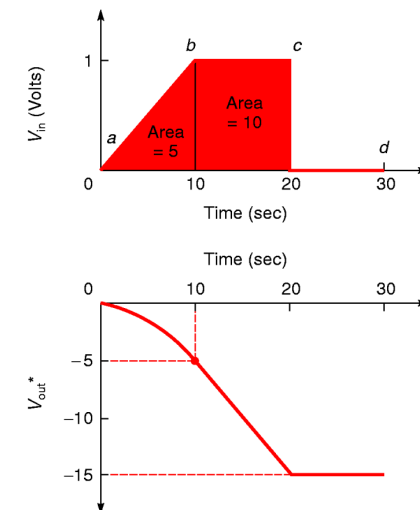Output of an Integrator Circuit ($RC = 1$)

e043.eps

OP-Amp: Differentiator

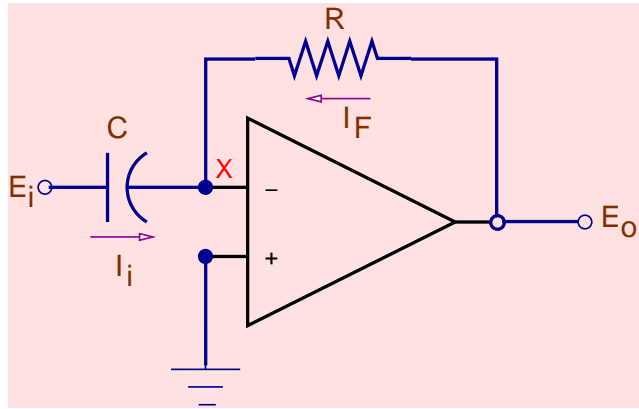


$$I_i = C \frac{dE_i}{dt}, \quad I_F = C \frac{E_o}{R} \quad \& \quad I_i + I_F = 0 \text{ (KCL)}$$

$$E_o = -RC \frac{dE_i}{dt}$$

x015.eps




OP-Amp: Differentiator & Integrator

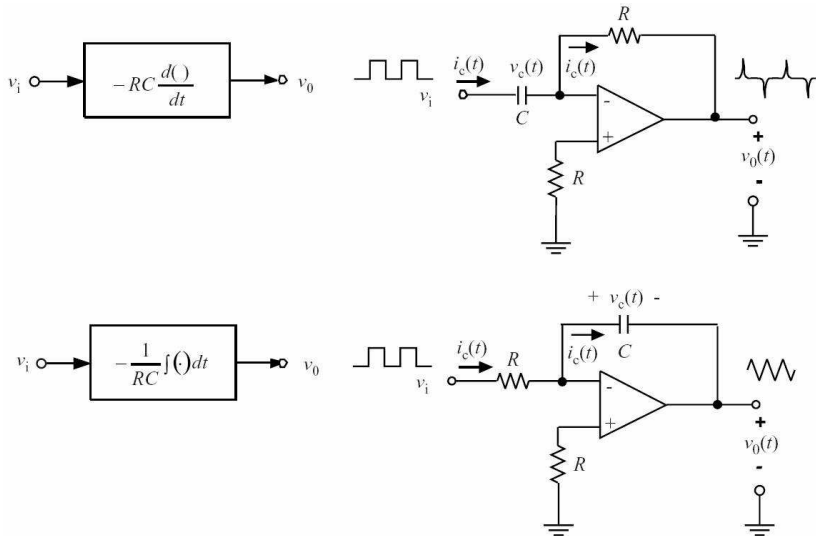

e428.eps




Output of a Differentiator Ckt. (RC = 1)

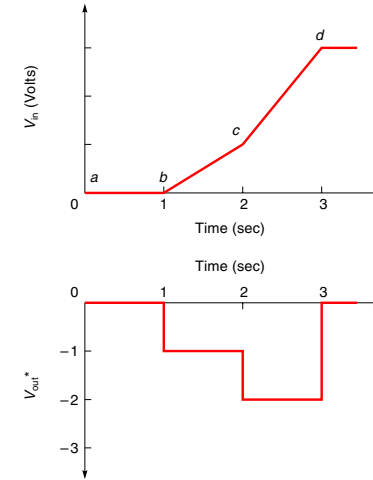

e044.eps




OP-Amp: Proportional Controller

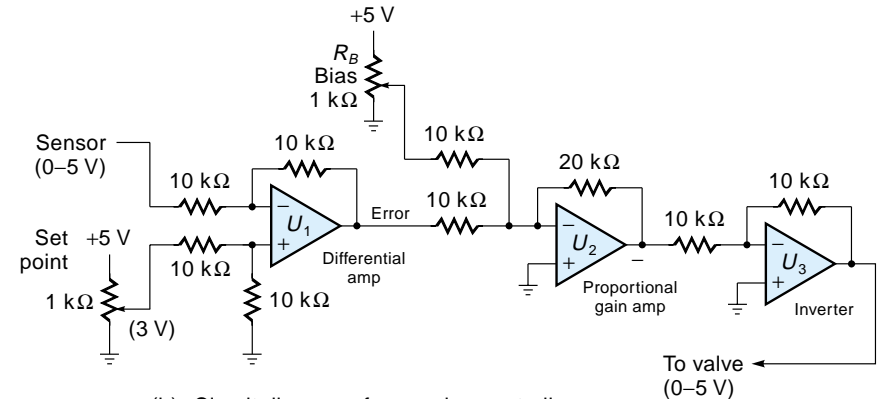

e180.eps




OP-Amp: PID Controller

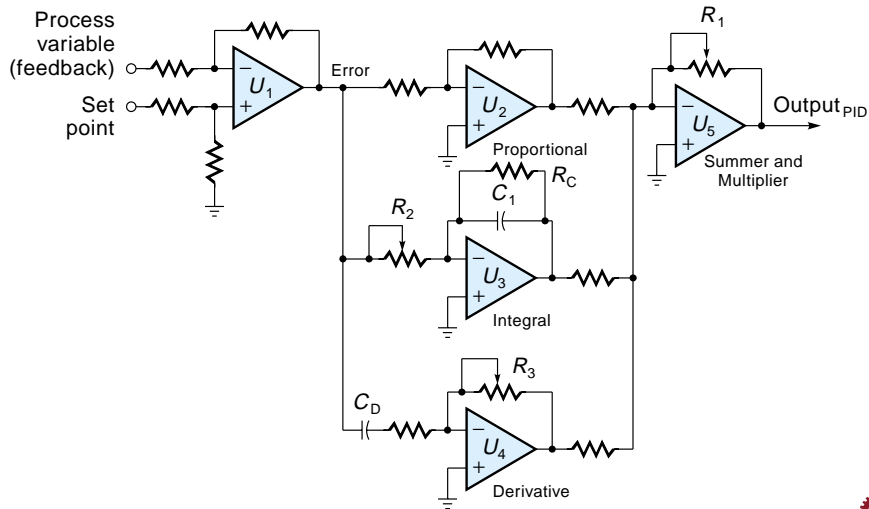

e181.eps



OP-Amps: Current Source

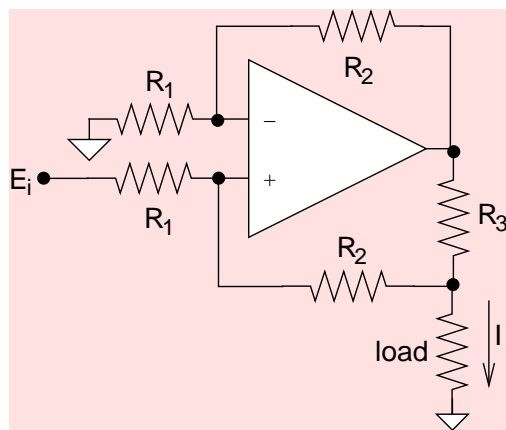


$$I = E_i \left(\frac{R_2}{R_1 R_3} \right)$$

if $R_2 \gg \text{load}$.

x017.eps



OP-Amp: Sample and Hold Circuit

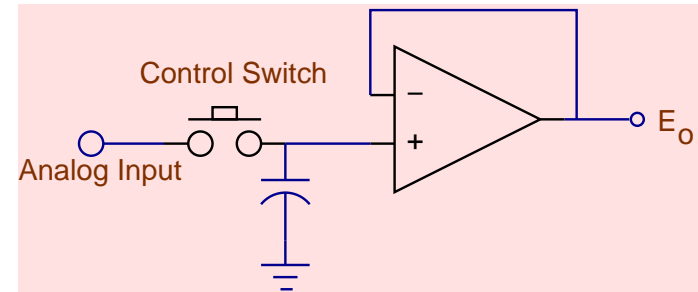


x016.eps

- S/H amplifier holds an analog value, until an A/D converter is ready to convert it to digital.
- The basis circuit consists of an electronic switch to the sample, with a capacitor for the hold and an op-amp voltage follower.




Low-Pass Filter Circuit

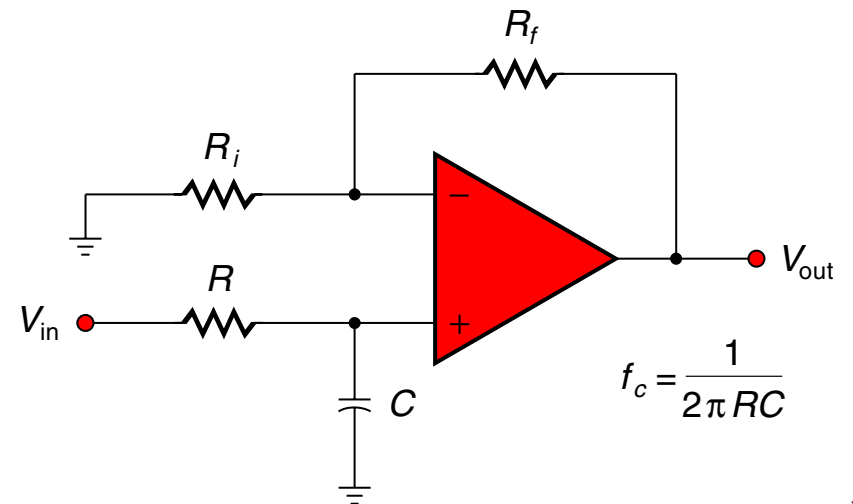

e101.eps



High-Pass Filter Circuit

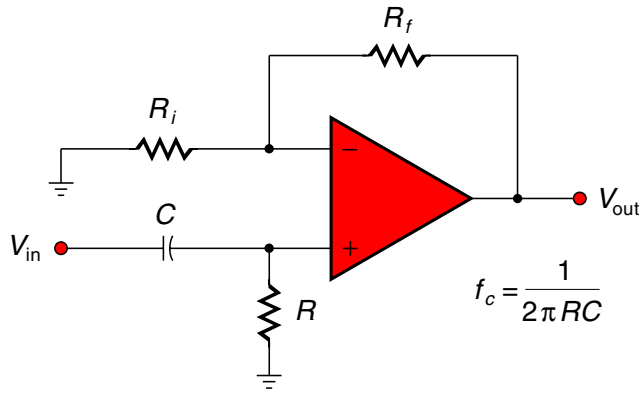


e102.eps



Band-Pass/Band-Reject Filter Circuits

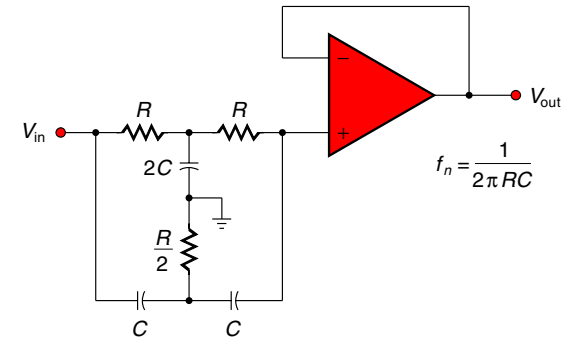- **Band-Pass Filter** - A band-pass filter can be built by cascading a low-pass filter and a high-pass filter together. The cut-off frequency of the low-pass filter must be higher than the cut-off frequency of the high-pass filter.
- **Band-Reject Filter** -



e103.eps

