

# Programmable Logic Controller

Dr. Md. Zahurul Haq, *Ph.D., CEA, FBSME, FIEB*

Professor  
Department of Mechanical Engineering  
Bangladesh University of Engineering & Technology (BUET)  
Dhaka-1000, Bangladesh

zahurul@me.buet.ac.bd  
<http://zahurul.buet.ac.bd/>

*Programmable Logic Controller (PLC) & VFD Workshop  
for Industrial Automation*



## Overview

- ① PLC Features
- ② PLC Basic Components & Operations
- ③ PLC Programming
- ④ Examples of Basic of PLC Operations
- ⑤ PLC Troubleshooting



# PLC Features

A **programmable logic controller (PLC)** is an industrial grade computer that is capable of being programmed to perform control functions. PLC has eliminated much of the hard-wiring associated with conventional relay control circuits.

- Rugged design,
- Industry standard I/O interfaces,
- Industry standard programming languages,
- Robust timing, counting and switching operations,
- Field programmable,
- Reduces hard wiring and wiring cost,
- Monitoring, error checking and diagnostics capability,
- Competitive in both cost and space requirements.



## PLC Features



T1619




T1620





1. Power supply
2. PLC (programmable logic controller)
3. Digital input cards
4. Digital output cards
5. Analog input cards
6. Transient surge protectors
7. Circuit breakers
8. Relay switches
9. Operator interface terminal
10. NEMA 12 enclosure

*Typical PLC control panel enclosure.*

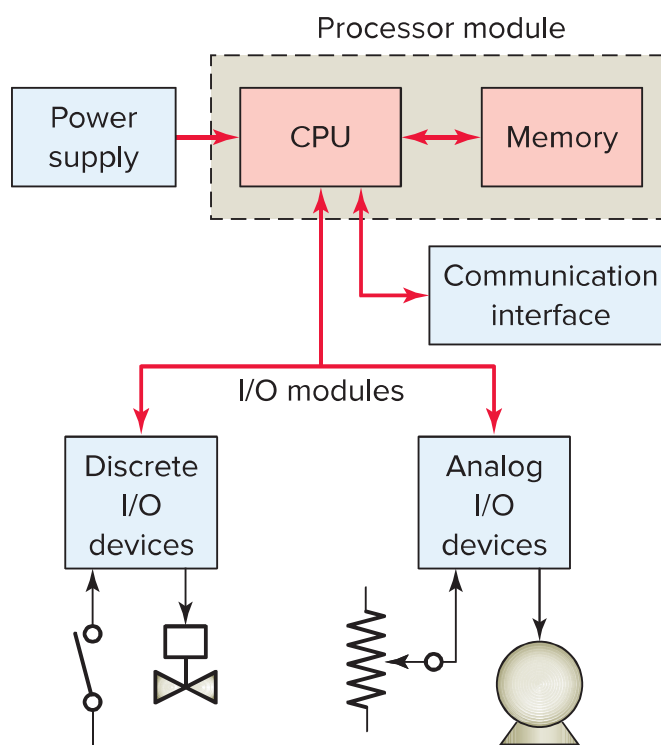

*PLC key components*



## Considerations in Choosing PLC

- Number and Types of **input & output** points required
- Size and type of **memory** required
- Speed and power required of **CPU** and instruction set
- **Manufacturer's support** and backup




## Basic Components

PLC is a microcomputer tailored specifically for certain control tasks.


- **Hardware**: consists of the actual device technology.
- **Firmware**: is the software part, known as *executive software*, that is permanently installed and supplied by the the PLC manufacturer. Executive software determines
  - what functions are available to the user's program,
  - how the program is solved,
  - how the I/O is serviced,
  - what the PLC does during power up and down and fault conditions.
- **Software**: is the user program. User programs are usually stored in the RAM.



# Key Components of a PLC

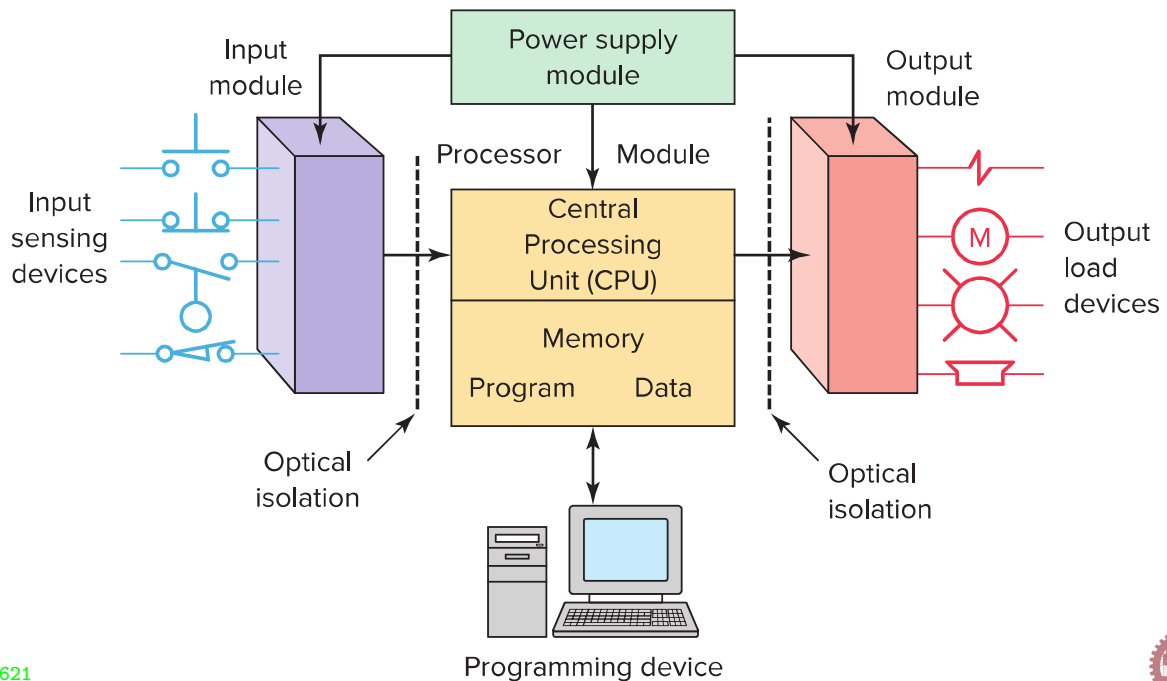

T1621

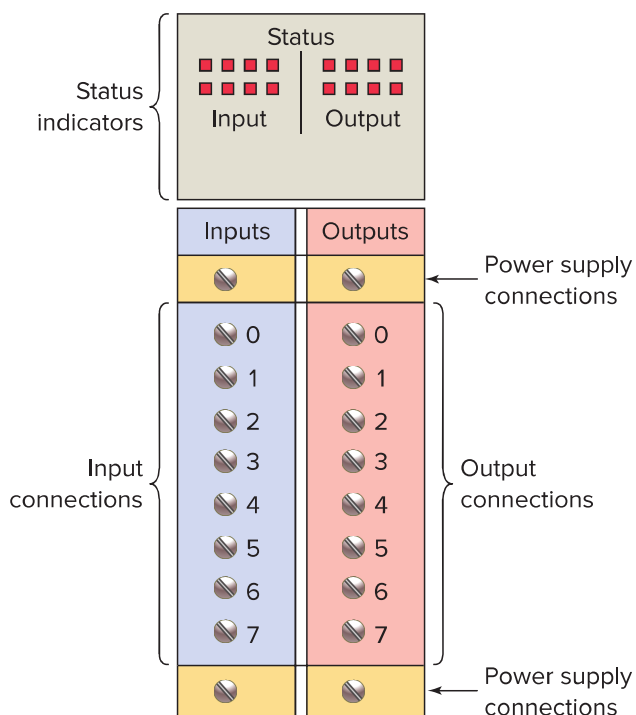


T1629




*Typical combination I/O module.*



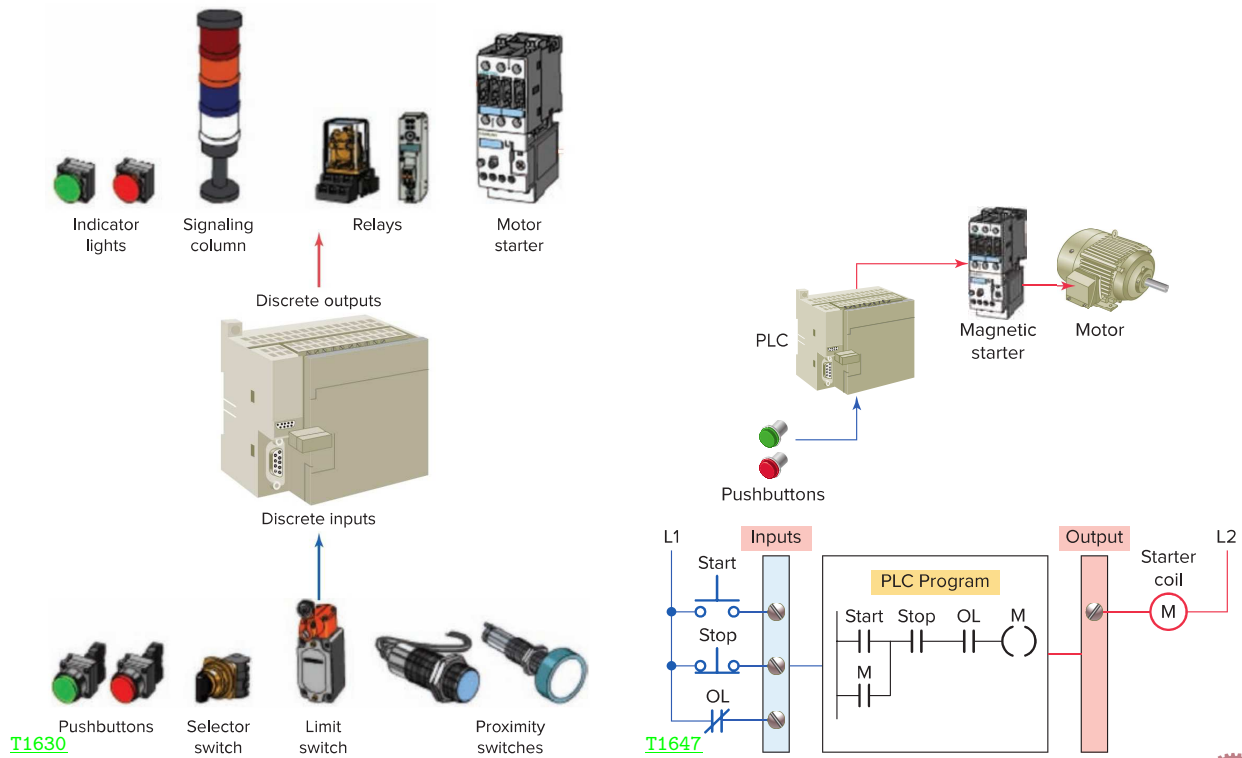


*Discrete input and output devices.*


*PLC control of a motor.*

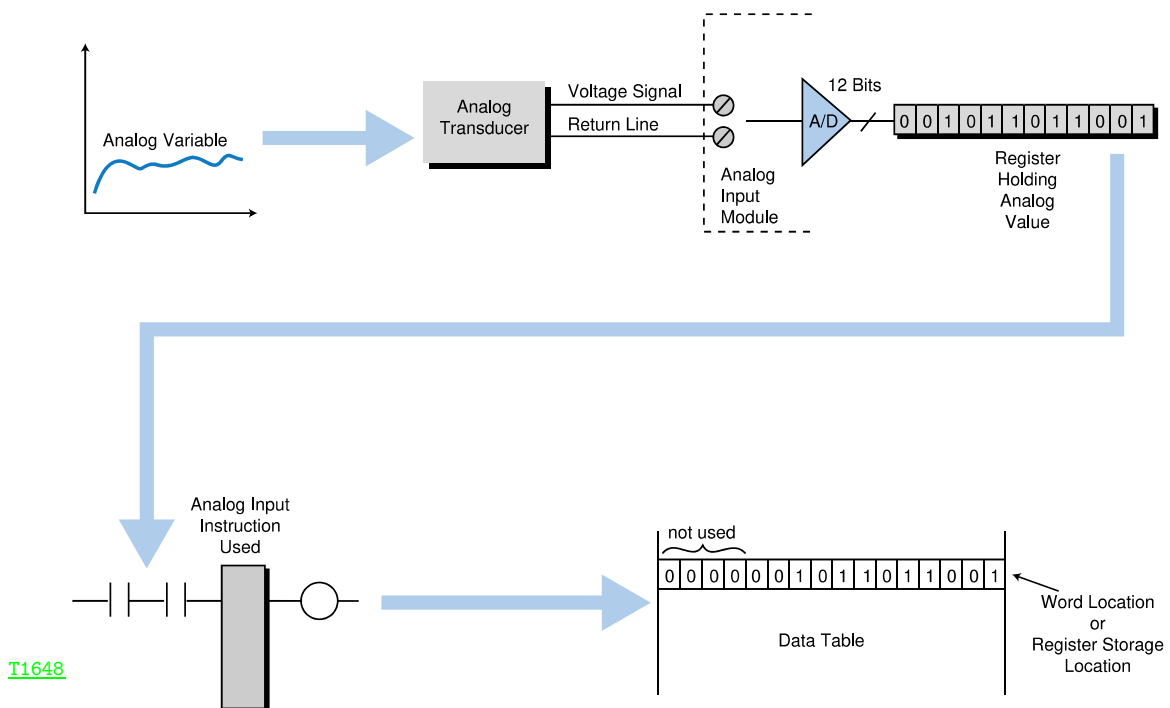

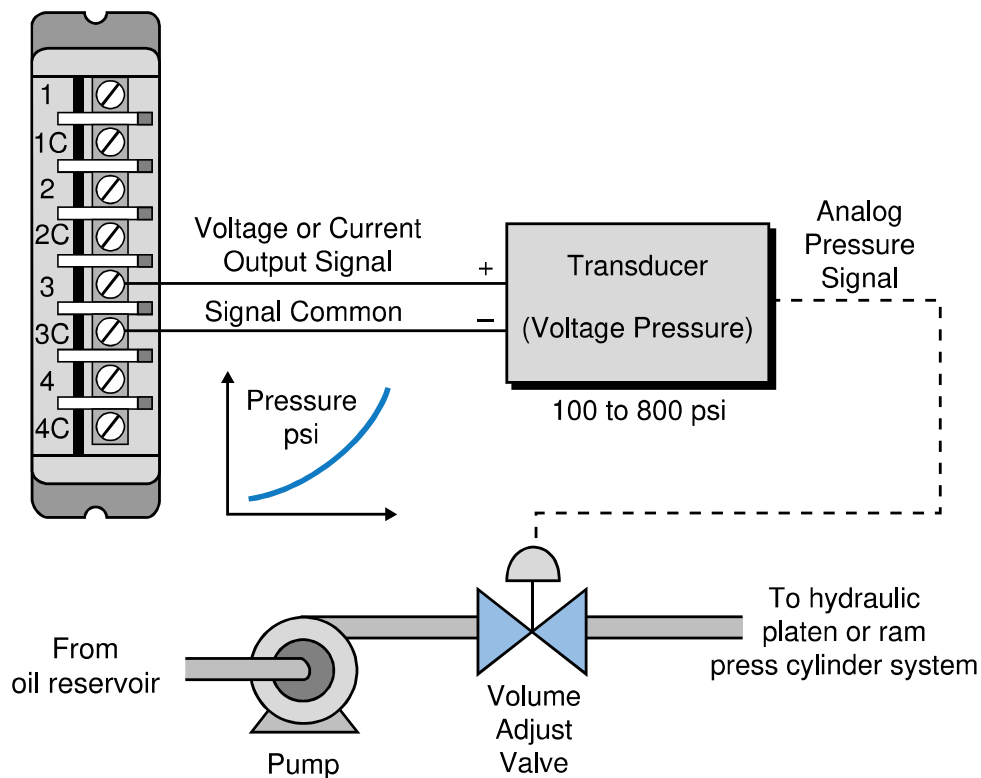*Process for inputting analog data to a word location.*



T1649

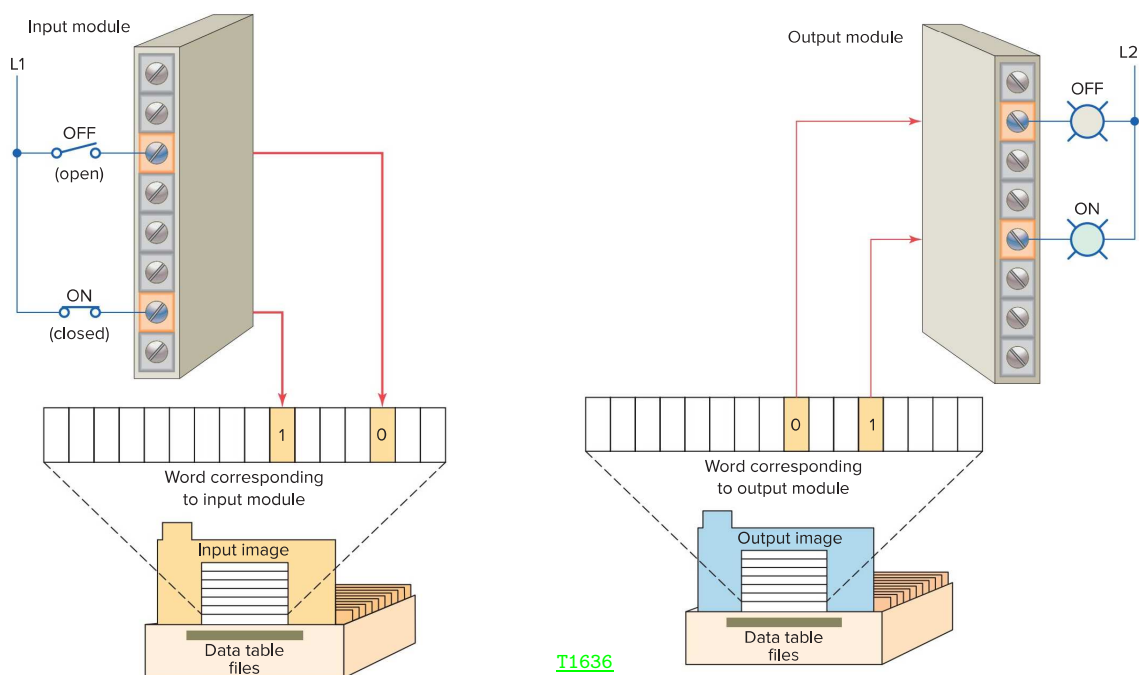*Volume adjustment.*

T1635


T1636

*Connection of an open and closed switch to the input image table file through the input module*

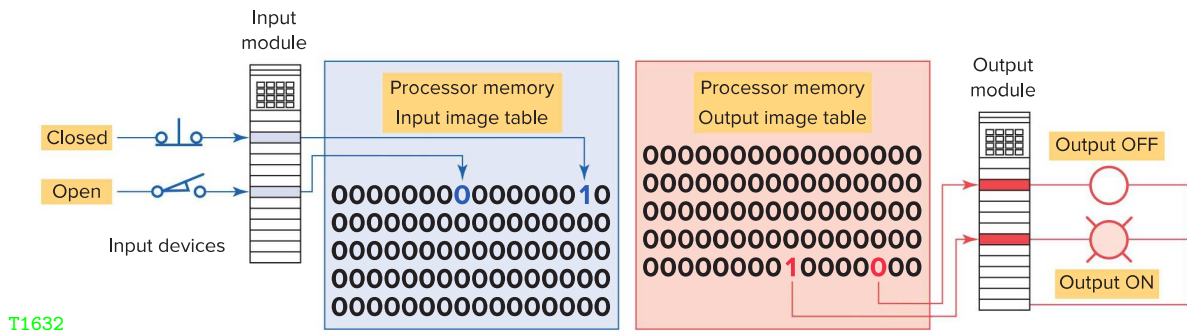
*Connections of pilot lights to the output image table file through the output module*








*Input and output tables.*

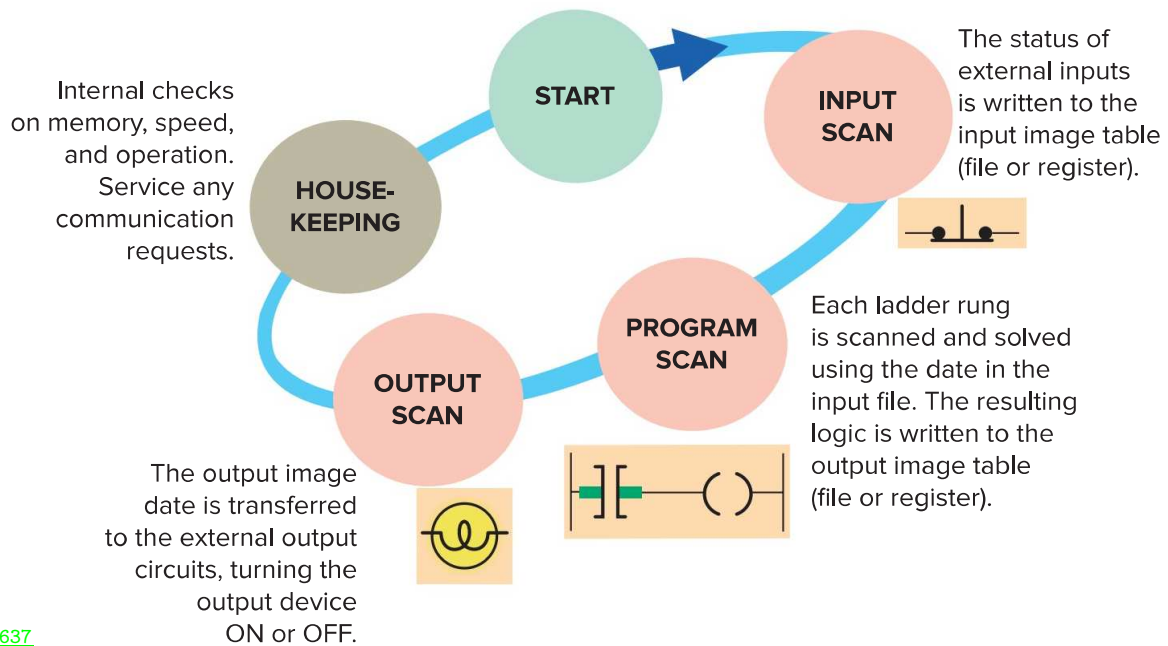


*PLC program scan cycle.*






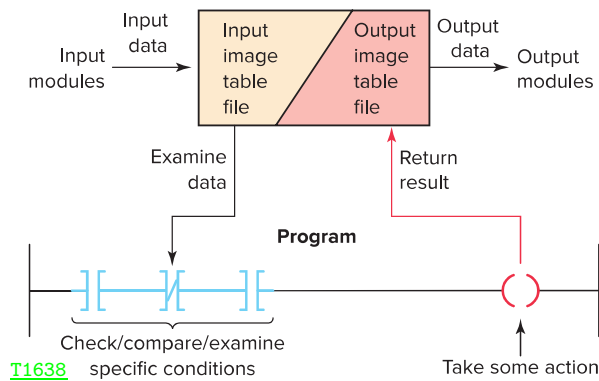

*Data flow during the scan process.*

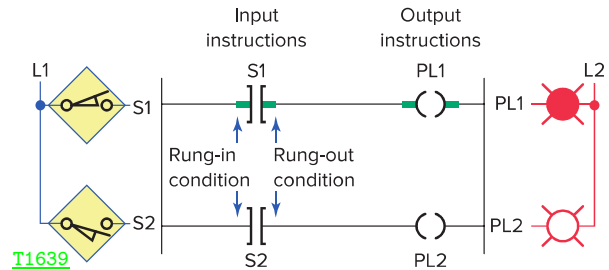

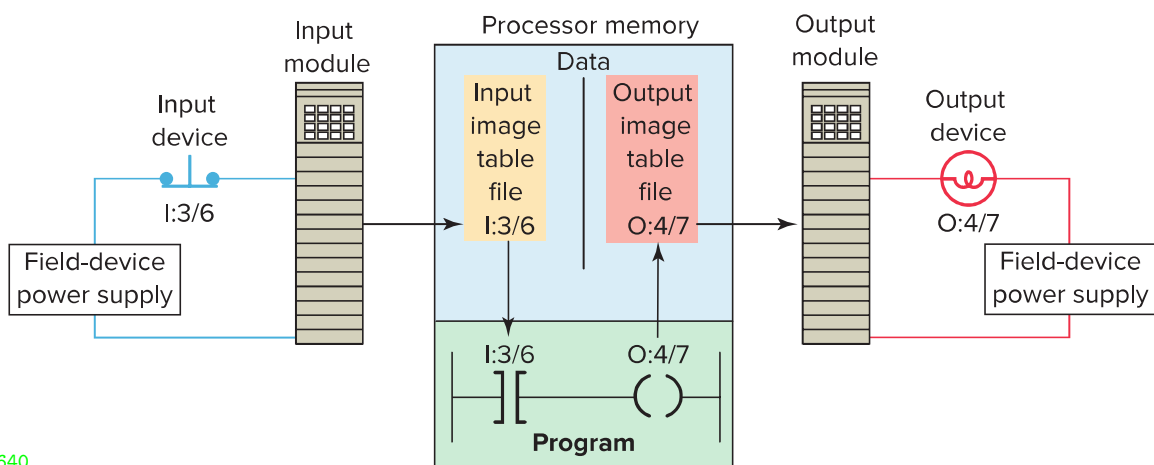*Evaluating ladder logic rung conditions.*




T1640


*Scan process applied to a single rung program.*



# PLC Programming

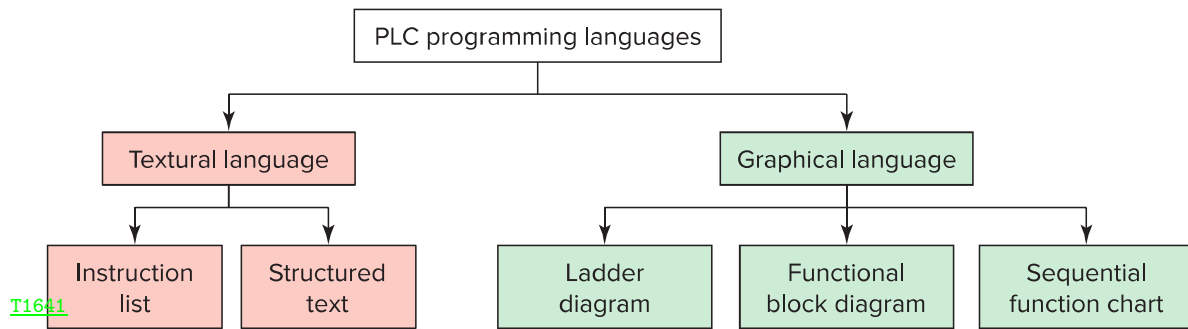

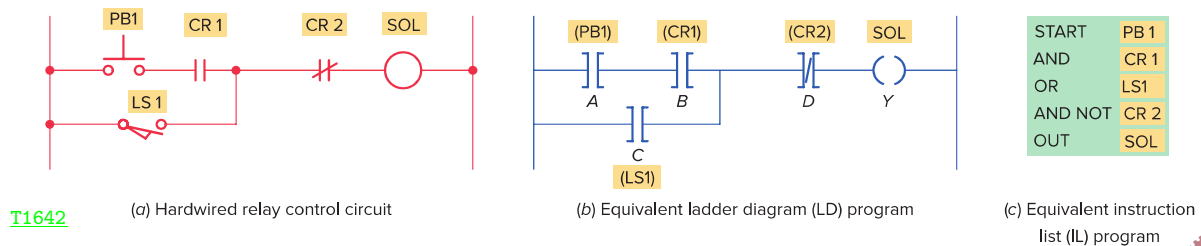*Standard IEC 61131 languages associated with PLC programming.*




*Comparison of ladder diagram and instruction list programming.*


## Typical PLC instruction

Instruction	Operation
XIC (Examine ON) . . . . .	Examine a bit for an ON condition
XIO (Examine OFF) . . . . .	Examine a bit for an OFF condition
OTE (Output Energize). . . . .	Turn ON a bit (nonretentive)
OTL (Output Latch) . . . . .	Latch a bit (retentive)
OTU (Output Unlatch) . . . . .	Unlatch a bit (retentive)
TOF (Timer Off-Delay) . . . . .	Turn an output ON or OFF after its rung has been OFF for a preset time interval
TON (Timer On-Delay). . . . .	Turn an output ON or OFF after its rung has been ON for a preset time interval
CTD (Count Down) . . . . .	Use a software counter to count down from a specified value
CTU (Count Up). . . . .	Use a software counter to count up to a specified value



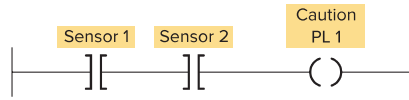


Ladder diagram

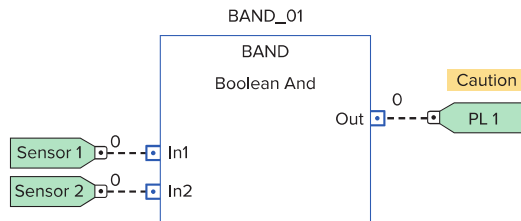

Function block diagram

T1643

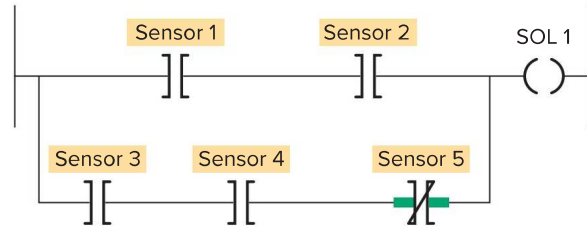

Ladder diagram (LD) program

```

IF Sensor_1 AND Sensor_2 THEN
    SOL_1 := 1;
ELSEIF Sensor_3 AND Sensor_4 AND NOT Sensor_5 THEN
    SOL_1 := 1;
END_IF;

```

Structured text (ST) program


T1644

*PLC ladder and equivalent function block diagram.*

*PLC ladder and equivalent structured text program.*



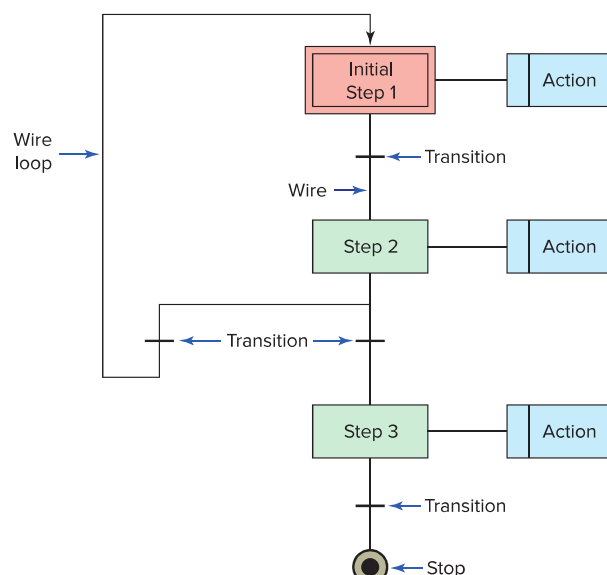Sequential function chart programming language is similar to process flowchart. SFC programming is designed to program more advanced processes. Program can be split into steps with multiple operations happening in parallel branches.



T1645

*Major elements of a sequential function chart program.*




# Programming Devices

Programming a PLC involves 3 categories:

- ① **Handheld Programmable** - are small inexpensive devices. These typically have membrane keys for entering data and LCD displays to show one line of a ladder program.
- ② **Dedicated Terminals** - are designed for one particular brand of PLC. These provides troubleshooting operation while the PLC is running.
- ③ **Micro-Computers / PCs** - are widely used to program and simulate the program. Tested programs are downloaded to the PLC using serial communications.




## PLC Programming

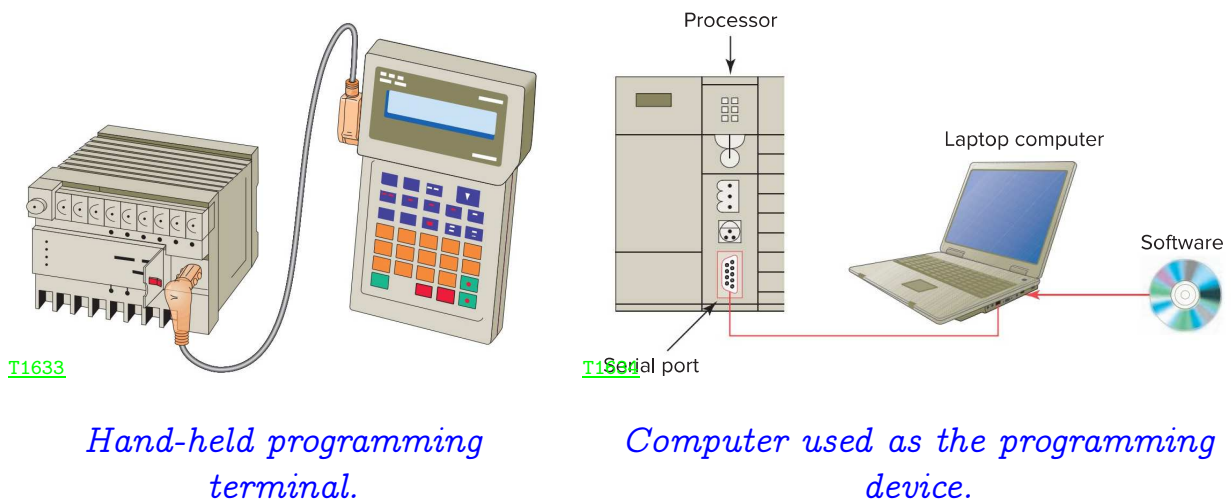


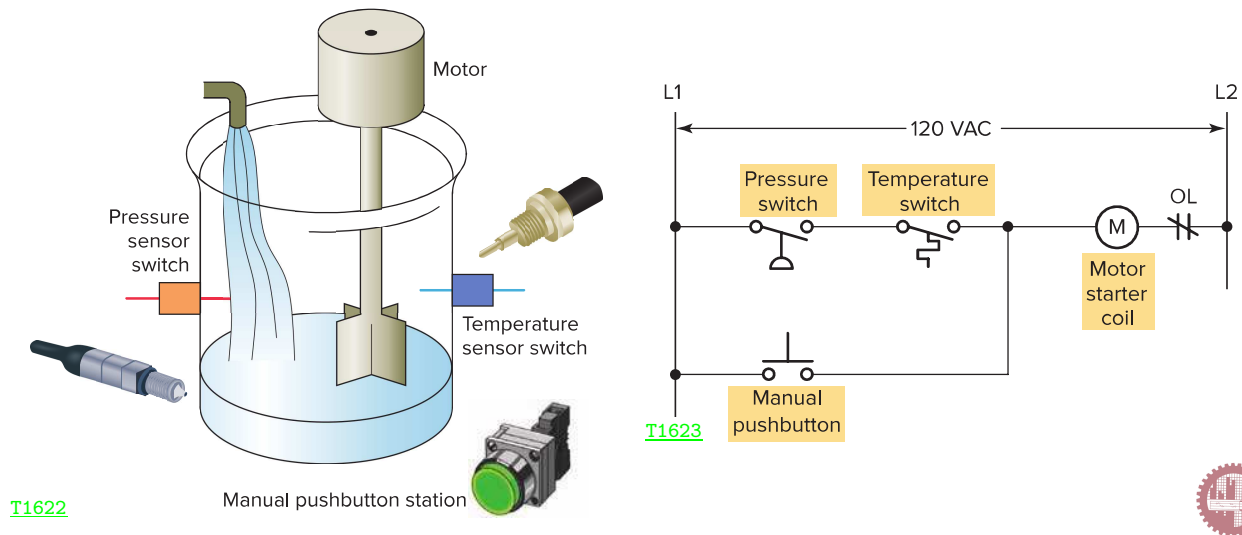
## Example: A Mixing Process

A mixer motor is to be used to stir the liquid in a vat when temperature and pressure reach pre-set values. Direct manual operation of the motor is provided by means of a separate push-button.




*Configured input module*

*Configured output module*

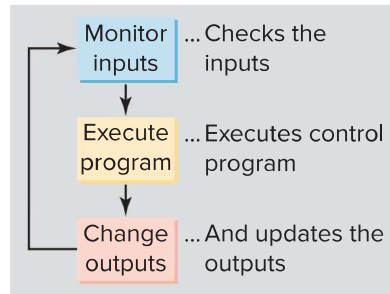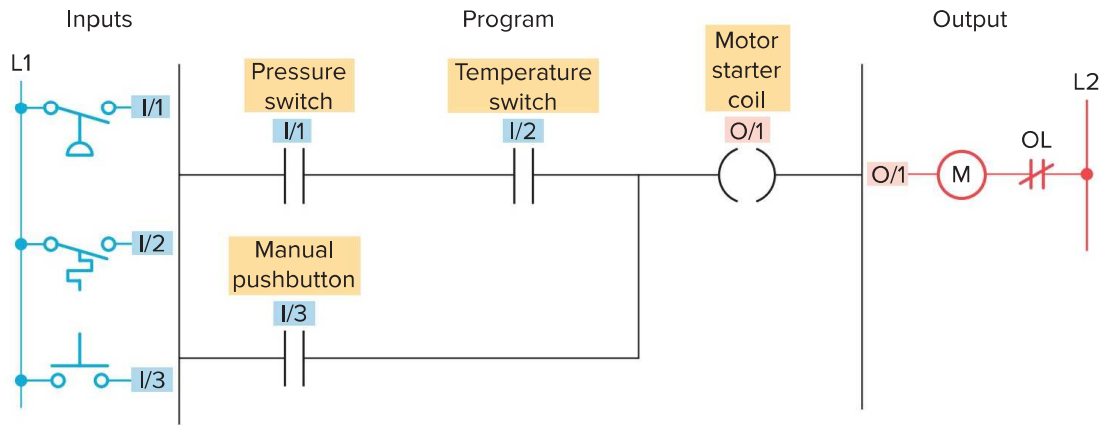

T1626

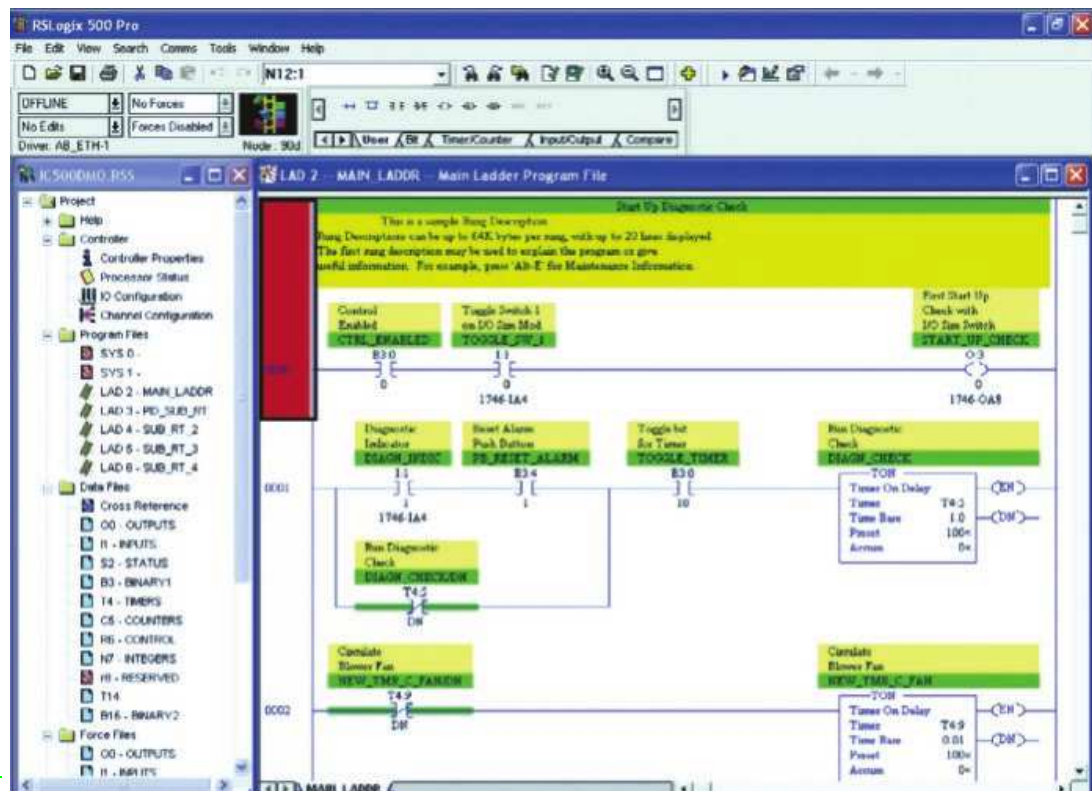Process control PLC ladder logic program with typical addressing scheme




T1627

Typical PC software used to create a ladder logic program
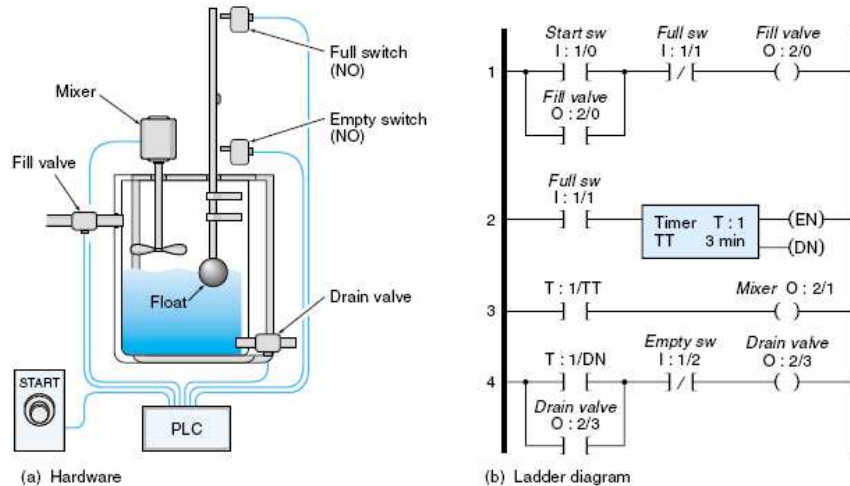
## Example: Batch Process using Timer


A batch process – filling a container with a liquid, mixing the liquid, and draining the container – is automated with a PLC. Steps:

- 1 a valve opens and lets the liquid into the container until it is full.
- 2 liquid in the container is mixed for 3 minutes.
- 3 a drain valve opens and drains the tank.




e197
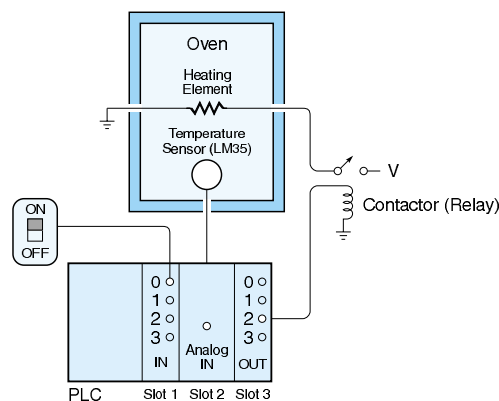
## Example: 2-point Controller in Oven at 100°C




e192

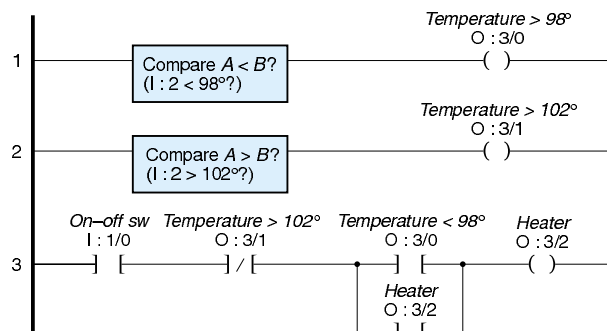

e193



# Input Trouble-shooting

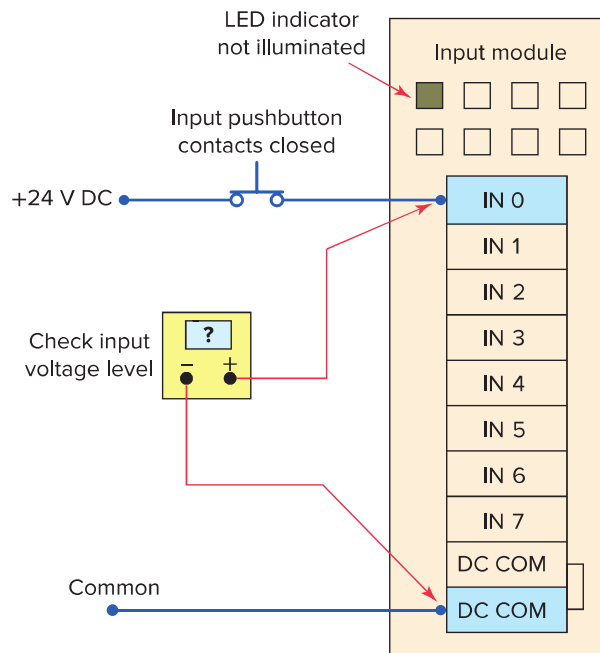

T1650

*Checking for input malfunctions.*



 

 

 
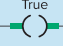



Input device troubleshooting guide				
Input device condition	Input module status indicator	Monitor display status indicator		Possible fault(s)
 Closed — ON 24 V DC input	ON	True 	False 	None - correct indications
 Open — OFF 0 V DC input	OFF	False 	True 	None - correct indications
 Closed — ON 24 V DC input	ON	False 	True 	Sensor condition, input voltage, status indicator are correct. Ladder instructions have incorrect indications. Input module or processor fault.
 Closed — ON 0 V DC input	OFF	False 	True 	Status indicator and instructions agree but not with the sensor condition. Open field device or wiring.
 Open — OFF 0 V DC input	OFF	True 	False 	Sensor condition, input voltage, status indicator are correct. Ladder instructions have incorrect indications. Input module or processor fault.
 Open — OFF 24 V DC input	ON	True 	False 	Input voltage, status indicator, and ladder instructions agree but not with sensor condition. Short circuit in the field device or wiring.

T1651



# Output Trouble-shooting

Output device troubleshooting guide			
Output device condition	Output module status indicator	Monitor display status indicator	Fault(s)
 Energized — ON	ON	 True	None - correct indication
 De-energized — OFF	OFF	 False	None - correct indication
 De-energized — OFF	ON	 True	Output instruction and status indicator agree but the field device does not. Open field device or wiring. Module circuit or fuse.
 Energized — ON	OFF	 True	Field device status and status indicator agree but the output condition does not. Module circuit or fuse.

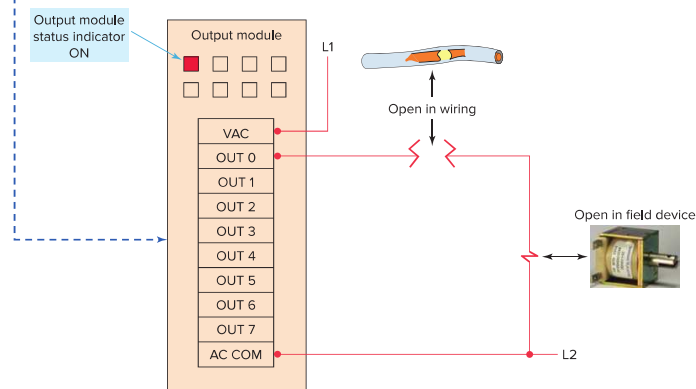

T1652

# Thanks a Lot!