

RME 3102: OP-AMP for Interfacing & Control

Dr. Md. Zahurul Haq, Ph.D., CEA, FBSME, FIEB

Professor
Department of Mechanical Engineering
Bangladesh University of Engineering & Technology (BUET)
Dhaka-1000, Bangladesh

<http://zahurul.buet.ac.bd/>

RME 3102: Advanced Mechatronics Engineering
Department of Robotics and Mechatronics Engineering,
University of Dhaka

<http://zahurul.buet.ac.bd/RME3102/>

Operational Amplifier (OP-amp)

Operational Amplifier (Op-amp)

OP-Amp is a low-cost and versatile IC (Integrated Circuit) consisting of many internal transistors, resistors, and capacitors. These are basic building blocks for:


- Amplifier
- Integrator and Differentiator
- Summer
- Comparator
- A/D and D/A converter
- Active filter
- Sample and Hold circuit
- ...etc.



OP-amp: Components


OP-amp has **Single Output** and **Two Inputs**:

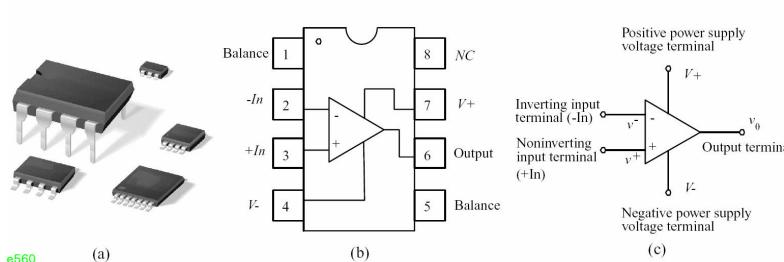- ① Noninverting input [+]: output is in phase with input.
- ② Inverting input [-]: output is 180° out of phase with input.



Operational Amplifier (OP-amp)

Internal Design of LM 741

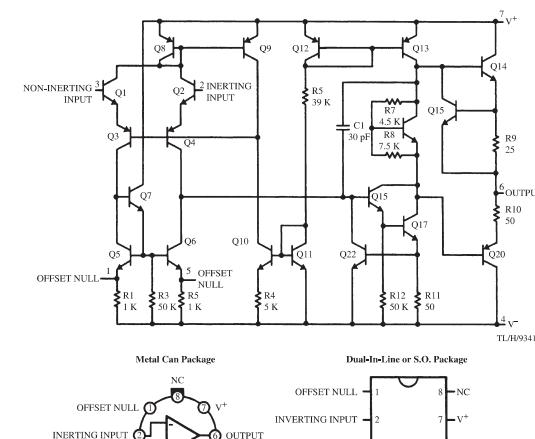

OP-amp: Equivalent Circuit

Rule 1. Infinite impedance at both inputs, $\Rightarrow I_+ = I_- = 0$
 Rule 2. Infinite gain, $\Rightarrow V_+ = V_-$
 Rule 3. Zero output impedance, $\Rightarrow V_{out} \neq f(I_{out})$

T1904

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 5 / 25

OP-amp: Voltage Comparator

In comparator circuit, there is no negative feedback, hence the circuit exhibits infinite gain and op-amp will saturate, i.e. output remains at the most positive or most negative output value.

T1905

T1906

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 6 / 25

Comparator Circuit: Application (ON-OFF Control)

T1907

Chatter is a practical problem, output voltage oscillates back-and-forth when input voltage is near to the threshold.

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 7 / 25

Window Comparator Circuit

T1908

Window Comparator is with inbuilt hysteresis; hysteresis means that switch-on voltage is greater than switch-off voltage.

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 8 / 25

OP-amp: Inverting Amplifier

T1909

At virtual ground:

- $I_{in} = I_f$ (Rule 1)
- $V_1 = V_2 = 0$ (Rule 2)
- $I_{in} \left(= \frac{V_{in}-V_1}{R_i} \right) = I_f \left(= \frac{V_1-V_{out}}{R_f} \right)$

$$\Rightarrow \boxed{\text{gain, } G \equiv \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}}$$

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 9 / 25

OP-amp: Noninverting Amplifier

T1910

- $I_{in} = I_f$ (Rule 1)
- $V_{in} = V_2 = V_1$ (Rule 2)
- $I_{in} \left(= \frac{V_{in}}{R_i} \right) = I_f \left(= \frac{V_{out}-V_{in}}{R_f} \right)$

$$\Rightarrow \boxed{G = 1 + \frac{R_f}{R_i}}$$

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 10 / 25

OP-Amp: Follower/Buffer

T1926

- In a noninverting amplifier with $R_i = \infty$ & $R_f = 0$:
 - Gain, $G = 1$, there is no voltage amplification.
 - This circuit is known as a **buffer** or **follower**.
- Buffer has a high input impedance and low output impedance. High input impedance effectively isolates the source from the rest of the circuit.

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 11 / 25

Op-amp: Voltage Follower Application

(a) Signal experiences voltage drop
(b) Equivalent circuit
(c) No signal voltage drop

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 12 / 25

Operational Amplifier (OP-amp)

Op-amp: Summing Amplifier

e179

T1911

$$V_{out} = -R_f \left[\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right]$$

If $R_a \neq R_b \neq R_c \dots$, V_{out} is a weighted sum of input voltages.

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 13 / 25

Operational Amplifier (OP-amp)

Summing Amplifier: Application

T1912

$$V_{out} = (V_t + V_h) \times 5$$

Example: Interface circuit for an air conditioning system

- when the sum of the voltages of temperature and humidity sensors goes above 1.0 V, &
- a threshold circuit in air conditioner require 5.0 V.

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 14 / 25

Operational Amplifier (OP-amp)

OP-amp: Differential Amplifier

T1913

$$V^- = V^+ \Rightarrow V_a \left[\frac{R_f}{R_a + R_f} \right] + V_{out} \left[\frac{R_a}{R_a + R_f} \right] = V_b \left[\frac{R_g}{R_b + R_g} \right]$$

$$V_{out} = V_b \left[\frac{R_g}{R_b + R_g} \cdot \frac{R_a + R_f}{R_a} \right] - V_a \left[\frac{R_f}{R_a} \right]$$

$$V_{out} = (V_b - V_a) \left[\frac{R_f}{R_a} \right] = c(V_b - V_a) \text{ if } \frac{R_f}{R_a} = \frac{R_g}{R_b} = c$$

© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 15 / 25





Operational Amplifier (OP-amp)

Instrument Amplifier

T1914

$$G = \frac{V_{out}}{V_b - V_a} = c = \frac{R_f}{R_a} = \frac{R_g}{R_b}$$

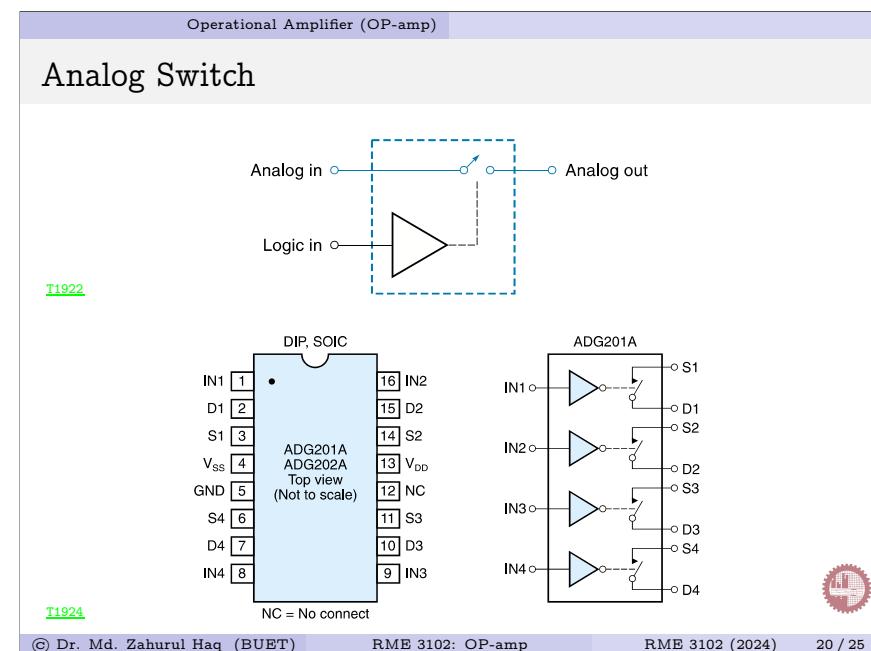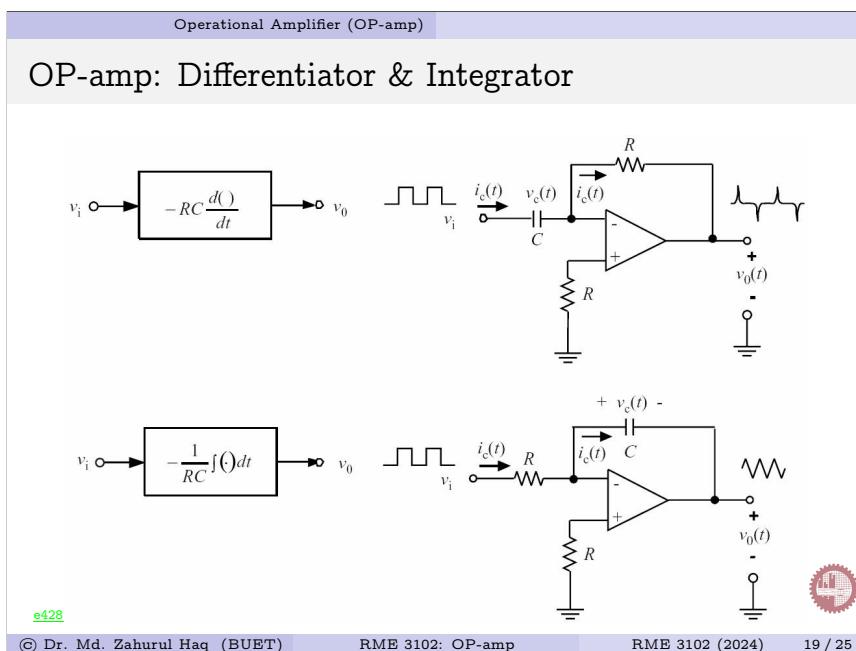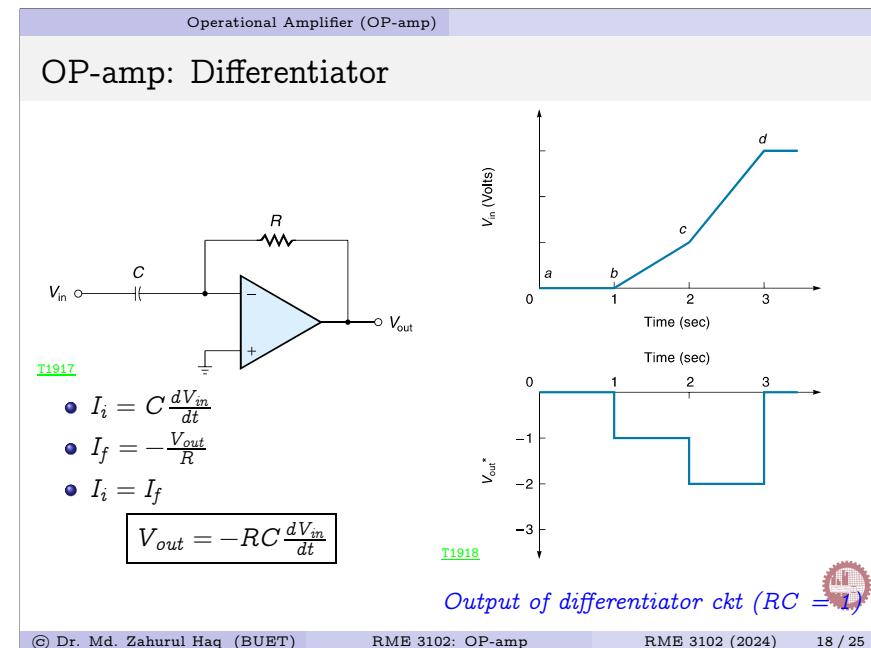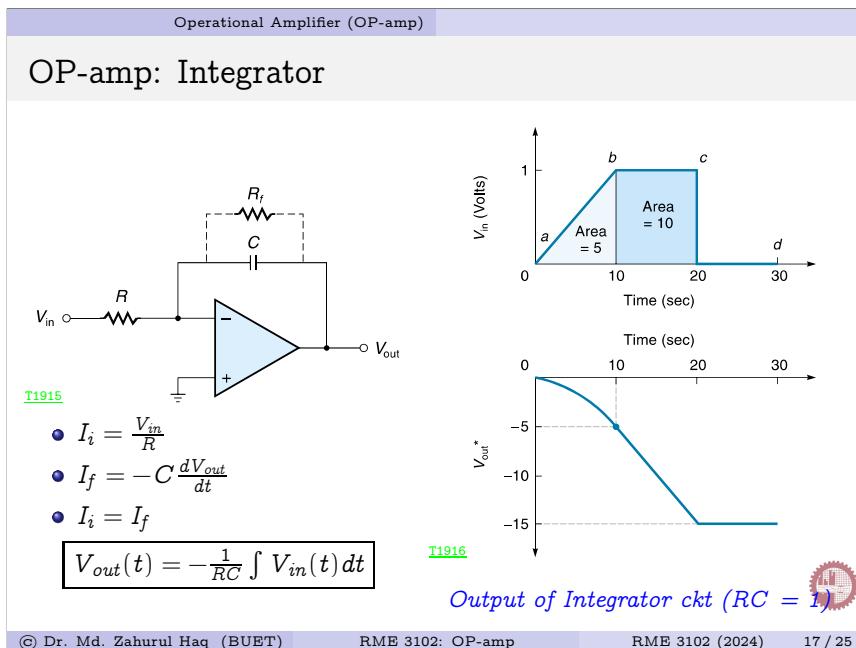© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 16 / 25




OP-amp: Sample and Hold Circuit

T1923

- S/H amplifier holds an analog value, until an A/D converter is ready to convert it to digital.
- The basic circuit consists of an electronic switch to the sample, with a capacitor for the hold and an op-amp voltage follower.

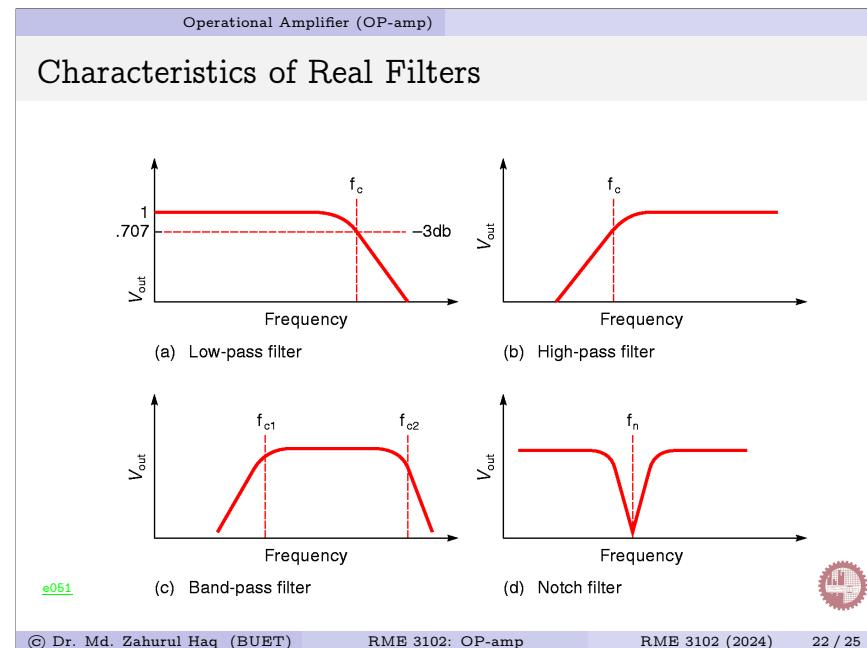© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 21 / 25



Operational Amplifier (OP-amp)

Low-Pass Filter Circuit

T1919

Band-pass Filter Circuit

T1925


High-Pass Filter Circuit

T1920

Band-reject Filter Circuit


T1921

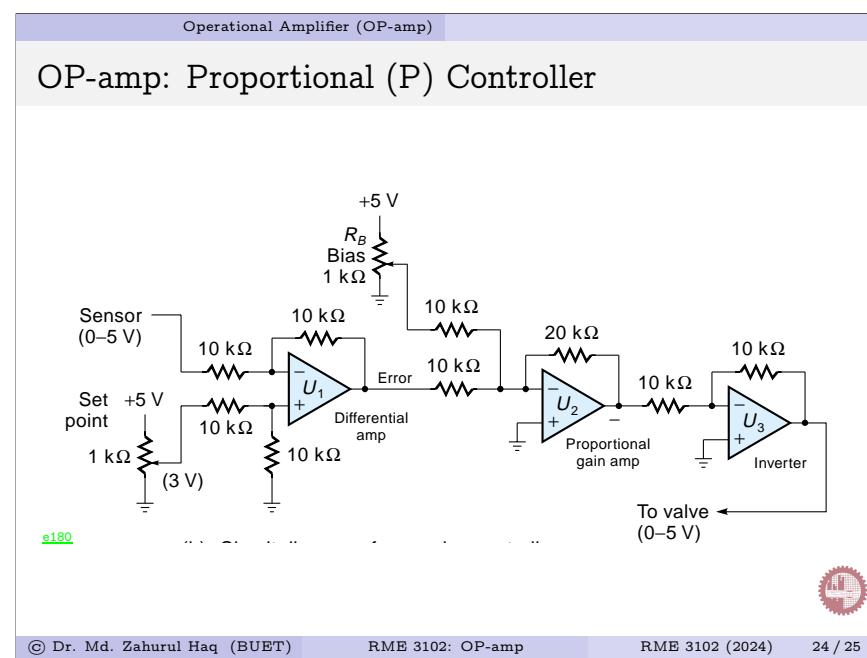© Dr. Md. Zahurul Haq (BUET) RME 3102: OP-amp RME 3102 (2024) 23 / 25



Operational Amplifier (OP-amp)

OP-amp: PID Controller

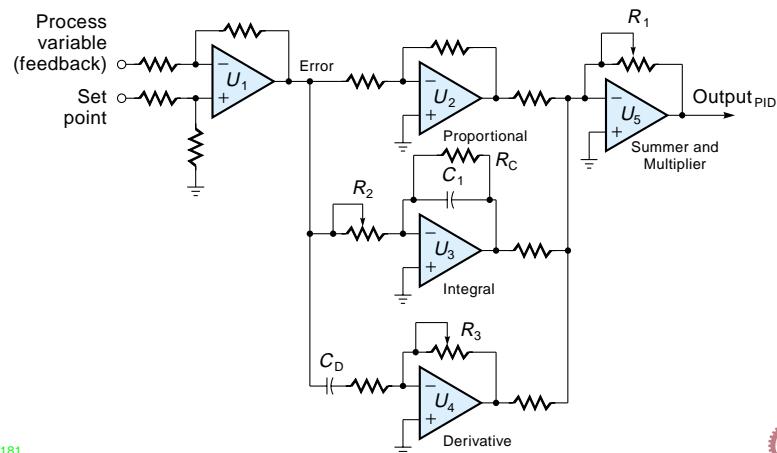

e181

